

17323

16172

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. **Attempt any TEN of the following:** **20**
- Define frequency and amplitude.
 - Define crest factor and form factor for sinusoidal A.C. waveform.
 - Draw impedance triangle for R-C series circuit. Write nature of power factor of this circuit.
 - Convert $Z = 6 + j8\Omega$ in polar form.
 - Define Q factor and write its expression.
 - Define admittance and state its unit.
 - Define balanced 3 phase load.
 - State the relation between line and phase values of voltage and current in 3 phase star connected system.
 - State Superposition Theorem.
 - State Thevenin's Theorem.
 - How to convert voltage source into equivalent current source?
 - State the behaviour of pure L at the time of switching.

P.T.O.

2. Attempt any FOUR of the following:**16**

- a) Derive the expression for current in pure capacitive circuit when connected to AC supply. Draw phasor diagram.
- b) Define :-
 - (i) Active Power
 - (ii) Reactive Power
 - (iii) Apparent Power
 - (iv) Power factor.
- c) Three identical impedances are connected in delta to a 3 phase, 400v. The line current is 35 Amp. and total power taken from supply is 15 KW. Calculate resistance and reactance of each phase.
- d) Compare the series and parallel resonant circuit.
- e) Define r.m.s. value and average value. An alternating voltage is $e = 200 \sin 314t$ Calculate its r.m.s. and average value.
- f) State any four advantages of polyphase circuits over single phase circuit.

3. Attempt any TWO of the following:**16**

- a) A resistance of 20Ω , an inductance of 0.2H and a capacitance of $100\mu\text{f}$ are connected in series across 220V , 50Hz supply. Determine
 - (i) impedance
 - (ii) current
 - (iii) active power
 - (iv) apperant power
- b) Two impedances $(12 + j16)$ and $(10-j20)\Omega$ are connected in parallel across a supply of $200\angle 60^\circ$ using admittance method calculate branch currents, total current and power factor of whole circuit.

- c) Using Nodal Analysis, find current in the 3Ω resistor for circuit A. Refer Fig. No. 1.

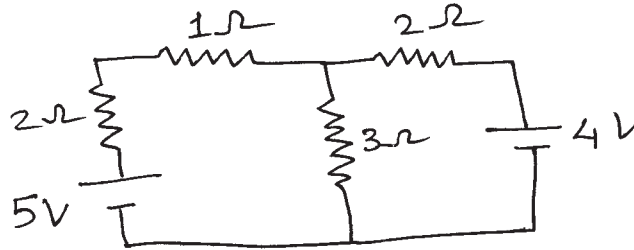


Fig. No. 1

4. Attempt any **FOUR** of the following: 16

- What is phase sequence? Draw waveforms of 3 phase emf.
- Derive the formulae for Delta to star transformation.
- A voltage $v = 100 \sin 314t$ is applied across a circuit containing 25Ω resistor and $80 \mu\text{F}$ capacitor in series. Determine
 - The expression for instantaneous current
 - Power consumed
- Three coils each with a resistance of 10Ω and inductance of 0.35 mH are connected in star to a 3 phase, 400V , 50Hz supply. Calculate line current and total power consumed.
- Explain lagging quantity and leading quantity explain this concept with voltage and current waveforms.
- Find current through 6Ω resistor using Mesh Analysis, for Circuit B. Refer Fig. No. 2.

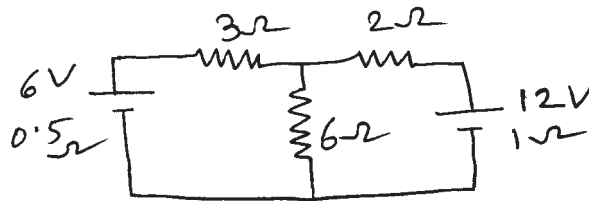
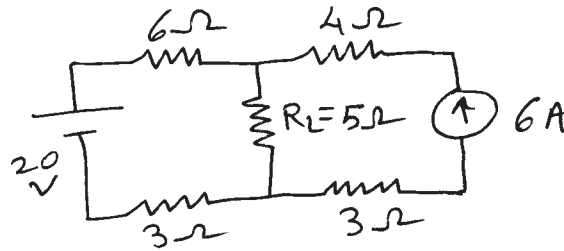


Fig. No. 2

5. Attempt any FOUR of the following:

16

- a) Derive the expression for resonant frequency in RLC series circuit.
- b) Draw the phasor diagram and waveforms of voltage and current in pure inductive circuit with single phase A-C supply.
- c) Using Norton's Theorem, find current through R_L in Fig. No. 3.


Fig. No. 3

- d) A series RLC circuit consisting of $R = 10\Omega$, $L = 0.1\text{H}$ and $C = 10\mu\text{F}$ is connected to 230V variable frequency supply. Calculate
- The frequency at which circuit behaves as purely resistive circuit.
 - Quality Factor.
- e) Derive the relation between line and phase current in 3 phase delta connected balanced load. Draw phasor diagram.
- f) Express
- $Z = 10\angle 60^\circ$ in rectangular form
 - $Z = 16 + j8$ in polar form.

6. Attempt any FOUR of the following:

16

- a) Calculate current through 5Ω resistor by using superposition theorem (Fig. No. 4)

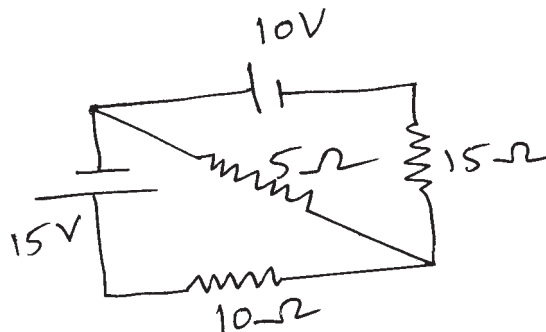Fig. No. 4

- b) Develop Thevenin's equivalent circuit between points A and B in Fig No. 5 and find current in $R_L = 10\Omega$.

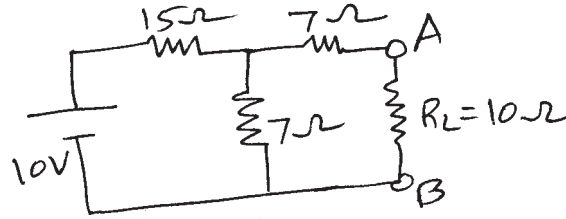


Fig. No. 5

- c) Find value of R_L in Fig. No. 6 for maximum power transfer.

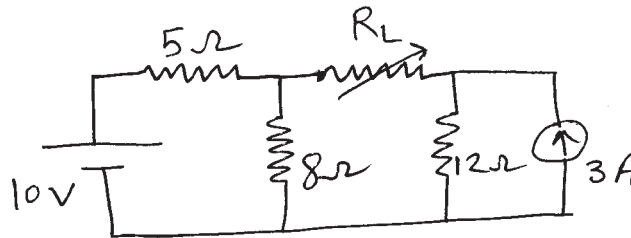


Fig. No. 6

- d) Explain the concept of Initial and final condition in switching circuit for L and C.
- e) Find voltages at nodes A and B in Figure No. 7.

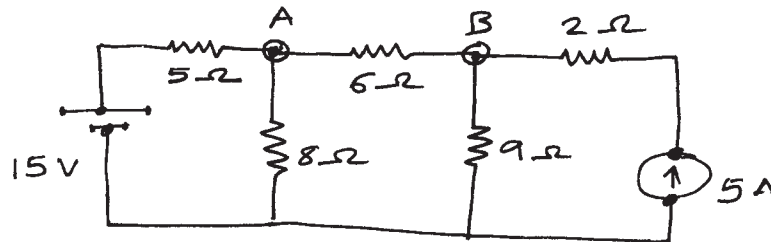


Fig. No. 7

- f) Explain how sinusoidal AC voltage is generated by using simple one loop generator.
