



17329

16172

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
 - (2) *Answer each Section on same/separate answer sheet.*
 - (3) *Illustrate your answers with neat sketches wherever necessary.*
 - (4) *Assume suitable data, if necessary.*
 - (5) *Use of Non-programmable Electronic Pocket Calculator is permissible.*
 - (6) *Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.*

Marks

SECTION – I

- | | |
|---|-------------------|
| 1. Attempt any nine of the following : | 18 |
| a) Define current and voltage with their units. | 2 |
| b) Give any two advantages of polyphase supply. | 2 |
| c) Define frequency and phase. | 2 |
| d) Draw speed torque characteristics of 3 phase induction motor. | 2 |
| e) List applications of auto transformer. | 2 |
| f) Write classification of electric drives. | 2 |
| g) State how the direction of rotation of 3 phase induction motor be reversed. | 2 |
| h) State the function of fuse. | 2 |
| i) State two types of earthing. | 2 |
| j) State two advantages of M.C.C.B. | 2 |
| k) Define voltage ratio and current ratio of transformer. | 2 |
| 2. Attempt any four of the following : | 16 |
| a) Define the following terms and its relation with amplitude. | 4 |
| a) R.M.S. value | b) Average value. |
| b) State the sequence of three phase supply, draw the phasor diagram of three phase supply. Write the equation of total power consumed in star and delta connected loads. | 4 |
| c) Define efficiency and voltage regulation of transformer. | 4 |
| d) Explain with suitable diagram working of universal motor. | 4 |
| e) State 4 factors considered for selection of motor in different drives. | 4 |
| f) State the necessity of earthing in electrical equipments. | 4 |

P.T.O.



- | | |
|---|-----------|
| 3. Attempt any four of the following : | 16 |
| a) Draw the construction diagram and explain the principle of operation of a single phase transformer. | 4 |
| b) Draw circuit diagram of direct on line starter. | 4 |
| c) What are the first aid measures taken when any person receives electrical shock ? | 4 |
| d) What are C.F.L. lamps ? What are its advantages ? | 4 |
| e) Explain the speed control of 3 phase induction motor by variable frequency drive with the help of block diagram. | 4 |
| f) Define the emf equations of transformer and state the meaning of each terms. | 4 |

SECTION – II

- | | | |
|---|-----------------------|----------------|
| 1. Attempt any nine of the following : | 18 | |
| a) Draw a symbol of photo diode and LED. | 2 | |
| b) State any four specification of photo transistor. | 2 | |
| c) Define α and β of the transistor. | 2 | |
| d) What is rectifier ? What are its types ? | 2 | |
| e) Define the term gain and band width of an amplifier. | 2 | |
| f) Convert the binary 110011 to decimal. | 2 | |
| g) State Barkhausens criteria of oscillations. | 2 | |
| h) Draw logic symbol and expression of AND and EX-OR gates. | 2 | |
| i) A full wave rectifier with capacitor filter employ $R_L = 50 \Omega$, $C = 1000 \mu\text{f}$. Calculate ripple factor. | 2 | |
| j) Draw dc load line of CE amplifier and define Q point. | 2 | |
| k) Perform the following conversion : | 2 | |
| i) $(212)_{10} = (?)_2$ | ii) $(436)_8 = (?)_2$ | |
| 2. Attempt any four of the following : | 16 | |
| a) Explain the circuit of transistor as a switch. | 4 | |
| b) Explain the working principle of LCD. | 4 | |
| c) What is filter ? State the need of filter. List different types of filters. | 4 | |
| d) Draw the circuit diagram of crystal oscillator and explain. | 4 | |
| e) Define line regulation and load regulation. | 4 | |
| f) Draw and explain RC phase shift oscillator. State its two application. | 4 | |
| 3. Attempt any four of the following : | 16 | |
| a) What is universal gate ? Design basic gates using NAND gates only. | 4 | |
| b) Draw circuit diagram of center tapped full wave rectifier. Explain its operation with waveforms. | 4 | |
| c) Give comparison between CE and CB configuration (any four points). | 4 | |
| d) Explain the working principle of LED. | 4 | |
| e) Draw the circuit of two stage RC coupled amplifier. Draw its frequency response. | 4 | |
| f) Draw the symbol and truth table of | 4 | |
| i) OR gate | ii) XNOR gate | iii) NOT gate. |