

22324

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.
  - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. Attempt any FIVE of the following: 10
- a) Define active power and reactive power for R-L-C series circuit.
  - b) Define RMS value and average value related to sinusoidal AC waveform.
  - c) Define term conductance and susceptance, state its unit.
  - d) Define - Phase sequence and write equations for instantaneous values of  $3\phi$  voltages.
  - e) Give equations for delta to star transformation.
  - f) State Norton's theorem.
  - g) State Reciprocity theorem.

P.T.O.

**2. Attempt any THREE of the following:** **12**

- a) Derive the expression for current in pure inductor circuit when connected to 1 $\phi$  AC Supply with graphical representation.
- b) Draw and explain RLC parallel Ckt. Find out the equation for resonant frequency.
- c) State any four advantages of polyphase circuit over single phase circuit. (system)
- d) Find the current in 6 $\Omega$  resistor in the circuit shown in Fig. No. 1 using mesh analysis.

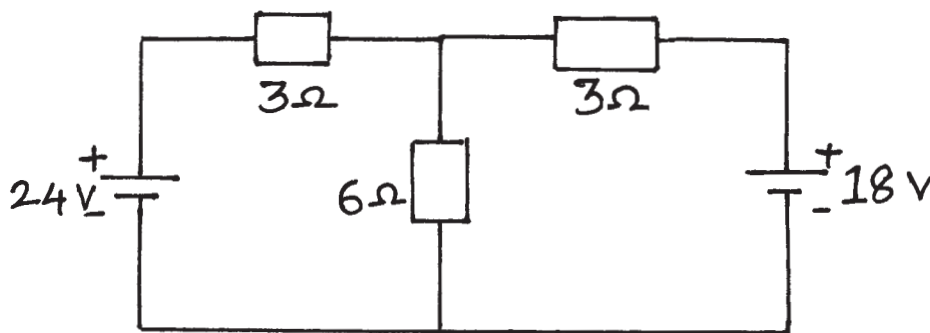


Fig. No. 1

**3. Attempt any THREE of the following:** **12**

- a) Derive the expression for resonance frequency for a RLC series circuit.
- b) Compare series resonance to parallel resonance on the basis of
  - i) Resonant frequency
  - ii) Impedance
  - iii) Current
  - iv) Magnification
- c) A star connected 3 $\phi$  load is supplied from 3 $\phi$ , 415V, 50 Hz supply. If the line current is 20 A and total power taken is 10KW, then determine
  - i) Load resistance and reactance per phase
  - ii) Load power factor
  - iii) Total 3 $\phi$  reactive power

- d) Find current in  $40\Omega$  and  $10\Omega$  in Fig. No. 2 using node voltage analysis method.

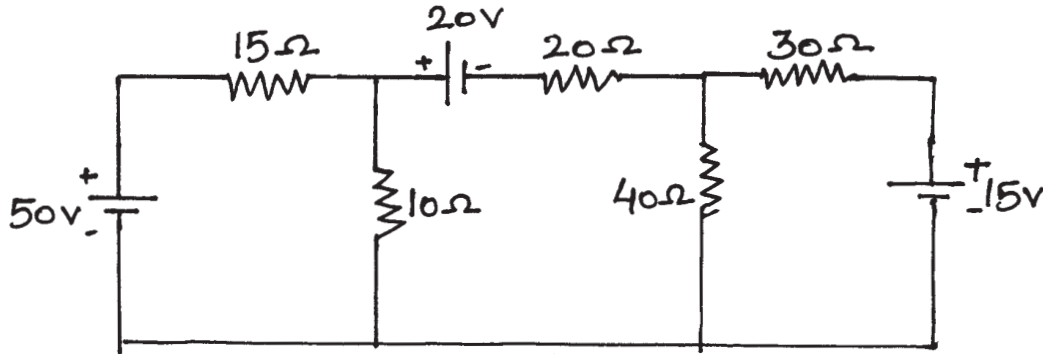


Fig. No. 2

- e) State Norton's theorem. Also write stepwise procedure for applying Norton's theorem to simple Ckt.

**4. Attempt any THREE of the following:**

12

- a) A R-L-C series circuit with a resistance of  $20\Omega$ , inductance of  $0.25\text{ H}$  and capacitance of  $100\mu\text{F}$  is supplied with  $240\text{ V}$  variable a.c. supply, calculate.
- Resonance frequency
  - Current at this condition
  - Power Factor
  - Quality Factor
- b) A choke coil has a resistance of  $2\Omega$  and an inductance of  $0.0035\text{H}$  is connected in parallel with  $350\mu\text{F}$  capacitor which is in series with a resistance of  $20\Omega$ . When the combination is connected across a  $200\text{ V}$ ,  $50\text{ Hz}$ .

Calculate

- Total current taken
  - P.F. of whole circuit
- c) Each phase of delta-connected load comprise a resistor of  $50\Omega$  and capacitor of  $50\mu\text{F}$  in series. Calculate the line and phase currents when the load is connected to a  $440\text{V}$ , 3 phase,  $50\text{ Hz}$  supply.

- d) Calculate the value of  $R$  which will absorb maximum power from the circuit of Fig. No. 3.

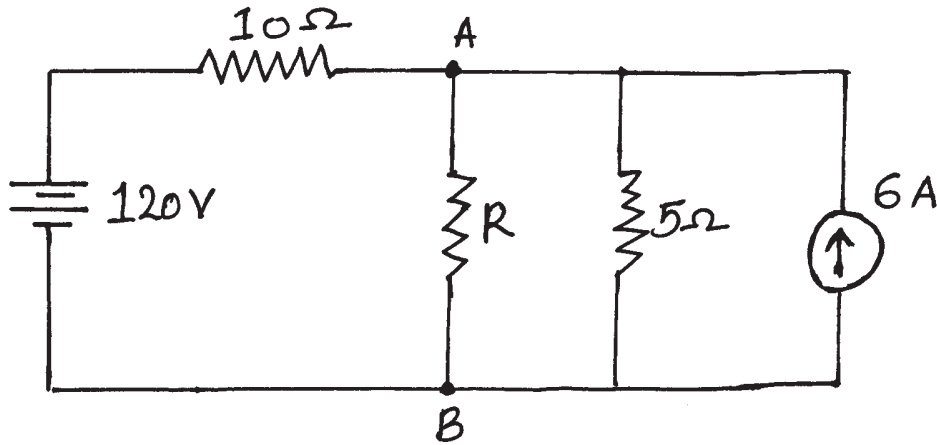


Fig. No. 3

5. Attempt any TWO of the following:

12

- a) A coil having resistance of  $10\Omega$  and inductance of  $0.15\text{H}$  is connected in parallel with R-C series combination having  $R = 5\Omega$  and  $C = 20\mu\text{F}$ . If supply voltage is  $110\text{V}$ ,  $50\text{Hz}$  then
- Draw circuit diagram
  - Calculate branch currents using impedance method
  - Power absorbed by the each branch
- b) Reduce the network shown in Fig No. 4 by applying Star/Delta or Delta/Star transformation and determine equivalent resistance ' $R_{AB}$ '.

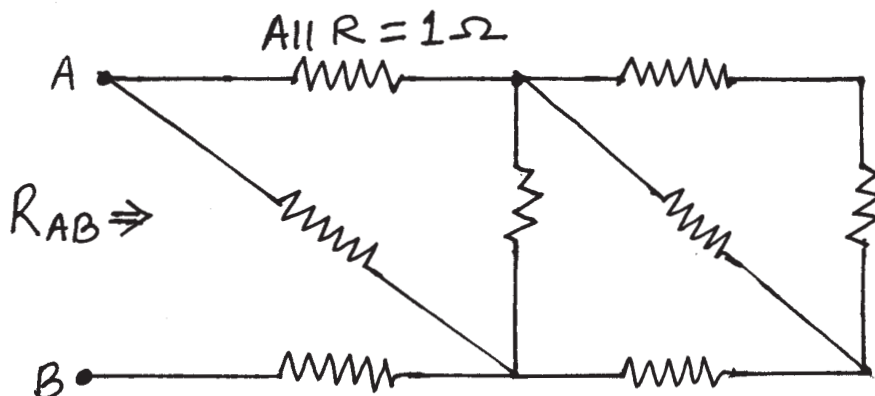


Fig. No. 4

- c) Find  $I_L$  for the circuit shown in Fig. No. 5 using superposition theorem.

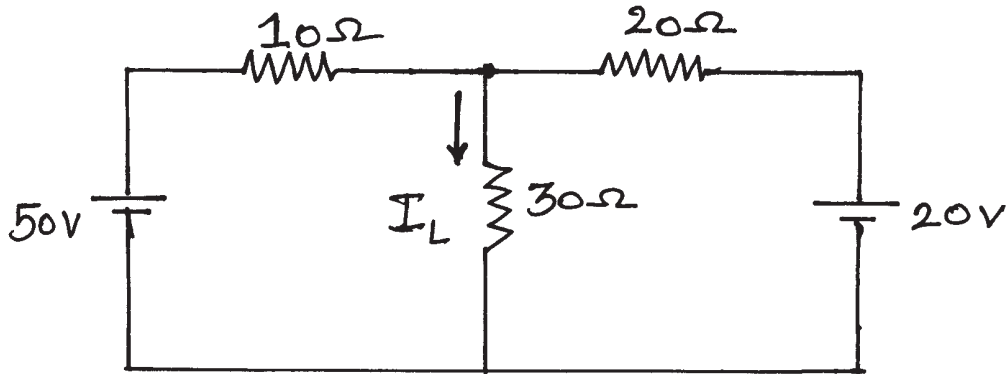


Fig. No. 5

6. Attempt any TWO of the following:

12

- a) An inductive coil  $(10+j40)\Omega$  impedance is connected in series with a capacitor of  $100\mu\text{F}$  across 230V, 50Hz, 1 $\phi$  Mains.

Find :

- Current through the circuit
  - P.F of the circuit
  - Power dissipated in the circuit.
  - Draw the phasor diagram.
- b) In a 3 Phase star connected system, derive the relationship  $V_L = \sqrt{3} V_{ph}$ .
- c) Apply superposition theorem to compute current  $I$  in the network shown in Fig. No. 6.

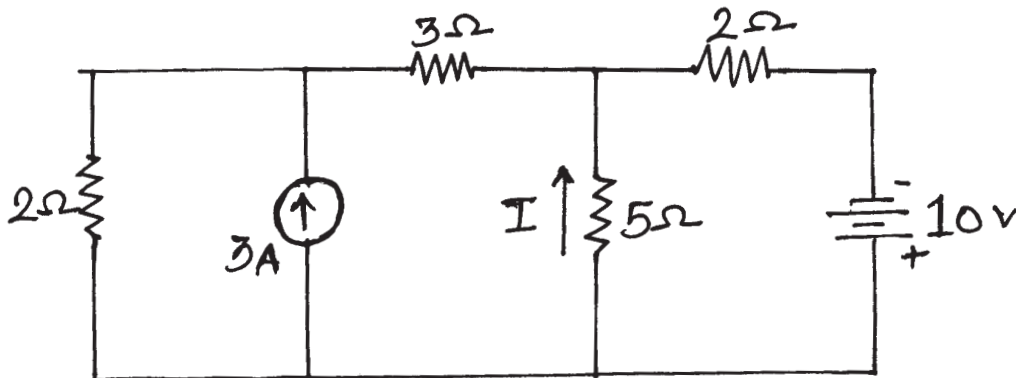


Fig. No. 6