

22329

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE of the following :

10

- (a) Define :
 - (i) Amplification
 - (ii) Bandwidth
- (b) Draw circuit diagram of transistor as an amplifier.
- (c) Define : Cross over distortion
- (d) State any two advantages of negative feedback.
- (e) Draw block diagram of negative feedback with its input and output waveforms.
- (f) Define : Time Base Generator
- (g) List two application of Switch Mode Power Supply (SMPS).

2. Attempt any THREE of the following :**12**

- (a) Define the following amplifier characteristics :
 - (i) Voltage gain
 - (ii) Current gain
- (b) Compare voltage series and voltage shunt feedback amplifier on following basis :
 - (i) Distortion
 - (ii) Output resistance
 - (iii) Bandwidth
 - (iv) Gain
- (c) Explain working of switch mode power supply with neat diagram.
- (d) With neat output waveform of sweep generator explain following terms :
 - (i) Retrace time
 - (ii) Sweep time

3. Attempt any THREE of the following :**12**

- (a) Compare Class A and Class B power amplifier on the basis of :
 - (i) Position of Q point
 - (ii) Distortion in output voltage
 - (iii) Efficiency
 - (iv) Power dissipation in transistor
- (b) List any four applications of power amplifier.
- (c) Draw +15V and – 15V dual polarity regulated power supply.
- (d) Draw pin configuration of adjustable voltage regulator IC LM 723 and state function of each Pin.

4. Attempt any THREE of the following :

12

- (a) Explain working of transformer coupled class A power amplifier with neat circuit diagram.
- (b) Explain working of FET as an amplifier with neat diagram.
- (c) Compare positive and negative feedback on basis of :
 - (i) Voltage gain
 - (ii) Distortion
 - (iii) Noise in output signal
 - (iv) Stability of circuit
- (d) Draw RC phase shift oscillator and explain how phase shift occurs.
- (e) Identify the circuit given below in Fig-1 and explain its working.

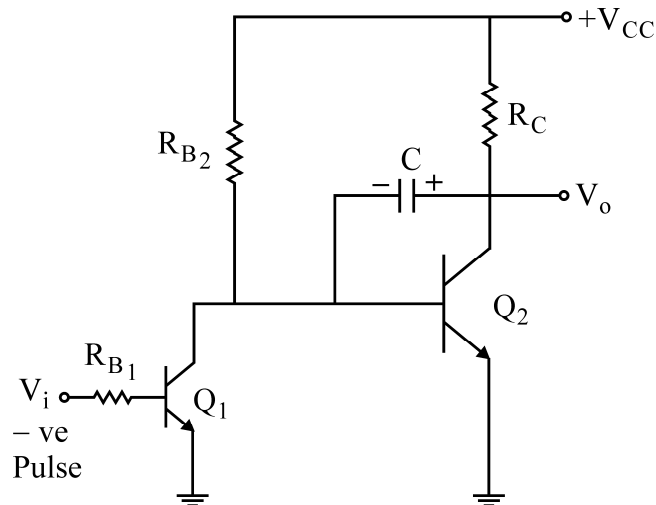


Fig.-1

5. Attempt any TWO of the following :

12

- (a) Draw circuit diagram and waveform of Bootstrap sweep generator.
- (b) Explain working of Class B power amplifier with neat diagram.
- (c) Draw circuit diagram of RC coupled transistor two stage amplifier and explain its working with its frequency response.

6. Attempt any TWO of the following :**12**

- (a) Sketch frequency response of single stage common emitter CE amplifier and label the following :
- (i) 3 dB lower cutoff frequency
 - (ii) 3 dB upper cutoff frequency
 - (iii) 3 dB bandwidth
- (b) Draw current series and current shunt feedback amplifier.
Compare them on the basis of :
- (i) Bandwidth
 - (ii) Voltage gain
- (c) Draw circuit diagram of Class AB Push Pull amplifier and list its any three advantages.
-