

22331

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. **Attempt any FIVE of the following:** **10**
- a) Define
- i) Accuracy
- ii) Precision
- b) State any two advantages of PMMC meter.
- c) Define resolution with respect to digital meter / instruments.
- d) List any four applications of CRO.
- e) State any two requirements of signal generator.
- f) Write two applications of function generator.
- g) Define error. Write the formula for percentage error.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) What is callibration? State important of callibration of instruments.
 - b) Draw the construction diagram of PMMC motor and explain the torque generation process.
 - c) Explain the operation of digital frequency motor with neat block diagram.
 - d) Describe working of Hay Bridge for measurement of inductance and Q of a coil.
- 3. Attempt any THREE of the following:** **12**
- a) Draw the circuit diagram of conversion of PMMC to multirange current meter. Derive equation for shunt resistance.
 - b) Draw the block diagram successive approximation type digital voltmeter and draw the output of SAR register verses time for $V_X = 6$ Volts (assume 4-bit SAR register or 4-bit ADC).
 - c) Draw the basic block diagram of single trace CRO. State materials is used for phosphor screen.
 - d) Compare series type and shunt type ohm-meters.
- 4. Attempt any THREE of the following:** **12**
- a) A basic D' Arsonval movement with an internal resistance of 50Ω and full scale deflection current of 2mA is to be as multirange voltmeter. Design the multirange voltmeter with range of $0-10\text{V}$, $0-50\text{V}$.
 - b) Design a multirange DC current meter using a basic movement having an internal resistance of 100Ω and full scale deflection current of $50\mu\text{A}$ and the ranges are $0-10\text{mA}$, $0-100\text{mA}$.
 - c) Draw the block diagram of logic analyzer. List the types of modes of display in it.

- d) Calculate the frequency of Channel-1 input for an oscilloscope which display the following Lissajous Fig. (Assume Channel-2 input frequency in 10KHz.)



Fig. No. 1

- e) A DVM is having $3\frac{1}{2}$ digit display
- Calculate the resolution.
 - Calculate the value displayed on DVM display for voltage, $V = 8.357$ Volts and the range of DVM selected is 0-10 Volts.

5. Attempt any TWO of the following:

12

- a) The expected value of the voltage across a resistor is 80V. However the measurement gives a value of 79V. Calculate
- Absolute error
 - % error
 - Relative accuracy
 - Percentage accuracy
- b) i) In a given bridge circuit, arms contain following constants-
- arm AB – $R = 1\text{ K}\Omega$,
 - arm BC – unknown coil,
 - arm CD – $R = 1\text{ K}\Omega$,
 - arm DA – $R = 470\Omega$ in parallel with $C = 0.22\ \mu\text{F}$
- and input supply frequency is 1KHz.
Calculate the unknown coil value.
- State the name of above bridge circuit.
 - State two applications of it.
- c) Describe function of the each block of spectrum analyzer with neat diagram.

22331

[4]

Marks

6. Attempt any TWO of the following:

12

- a) Give any six points of comparison between digital instrument and analog instrument.
 - b)
 - i) Draw the circuit diagram of half wave and full wave rectifier type AC voltmeters.
 - ii) State the sensitivity of each meter with respect to sensitivity of basic PMMC meter.
 - c) State any six specifications of CRO. State the phase measurement formula using CRO with necessary diagram.
-