

22216

21222

3 Hours / 70 Marks

Seat No.

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

15 minutes extra for each hour

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw the symbol of LED and Zener diode.
- (b) State types of JFET and draw its symbol with terminal names.
- (c) Define transistor & state its types.
- (d) State any two application of FET.
- (e) State the need of DC regulated power supply.
- (f) Define :
 - (i) Line regulation
 - (ii) Load regulation
- (g) Draw the forward bias characteristics of Silicon (Si) pn junction diode.

2. Attempt any **THREE** of the following :

12

- Compare pn junction diode and zener diode.
- Describe operation of voltage divider biasing with neat circuit diagram.
- Draw block diagram of DC regulated power supply and write function of each block.
- Explain the phenomenon of thermal runaway in BJT. Write the method to avoid it.

3. Attempt any **THREE** of the following :

12

- State the values of the following parameters with reference to full wave rectifier :
 - Ripple factor
 - Efficiency
 - TUF
 - PIV
- Draw circuit diagram and waveforms for full wave center tapped rectifier.
- Sketch input & output characteristics of CE configuration. Label various regions on it.
- Determine output voltage V_O , load current I_L , zener current I_Z & power dissipation in zener diode for the circuit shown below (Fig. – 1).

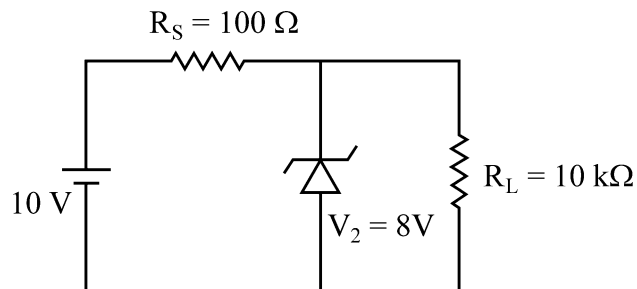


Fig. – 1

4. Attempt any THREE of the following :**12**

- (a) Compare L, C, LC and TT filters (any 4 points).
- (b) Explain working of NPN transistor with neat labelled diagram.
- (c) Compare CB, CE & CC configuration of transistor on the basis of any four factors.
- (d) A JFET has a drain current of 5 mA. If $I_{DSS} = 10 \text{ mA}$ & $V_{GS} \text{ (off)} = 6\text{V}$. Find the value of (i) V_{GS} (ii) V_P
- (e) With the help of reverse characteristics of zener diode explain its use as a regulator.

5. Attempt any TWO of the following :**12**

- (a) Draw & explain the drain & transfer characteristics of N-channel JFET.
- (b) An AC supply of 230 V is applied to HWR through a transformer with turns ratio of 10 : 1. Find average DC output voltage, output current and PIV of diode, also rms value of voltage & current.
- (c) Explain forward and reverse biased VI characteristics of PN junction diode.

6. Attempt any TWO of the following :**12**

- (a) Draw the construction of LED & write advantages, disadvantages and applications of it (each two points).
- (b) (i) In CE configuration if $\beta = 99$, leakage current $I_{CEO} = 50 \mu\text{A}$. If base current is 0.5 mA, determine I_C & I_E .
- (ii) Derive relation between α & β .

- (c) Identify the given circuits in figure 2 and draw input and output waveform for following circuit (Fig. - 2) :

