

22310

22223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each section on separate answer book.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

SECTION - I

1. Attempt any SIX of the following: 12
- Define permeability and reluctance.
 - Draw power triangle for AC circuit.
 - Define RMS value and average value.
 - State the relation between time period and frequency.
Calculate time period for 60Hz frequency.
 - List the application of single phase induction motor (any four)
 - List the different types of transformer.
 - List two applications of auto transformer.

P.T.O.

2. Attempt any THREE of the following: 12

- a) Compare electric circuit and magnetic circuit on any four points.
- b) Derive emf equation of single phase transformer.
- c) An alternating current is represented by $i = 50.5 \sin \left(314t + \frac{\pi}{2} \right)$
Calculate
 - i) Amplitude of current
 - ii) Frequency
 - iii) Phase difference
 - iv) RMS value of current
- d) State four major parts of transformer and give material used for each.

3. Attempt any TWO of the following: 12

- a) Related to electromagnetism induction
 - i) Define Faraday's both laws.
 - ii) Define self and mutually induced emf
 - iii) State equations of self and mutual inductance.
- b) List any four types of single phase AC motor. Draw neat circuit of any one type. Explain its working.
- c) Draw RL series circuit. Draw waveform and phasor diagram for the same. Write equation of current, voltage and power for this circuit.

SECTION - II

- 4. Attempt any FIVE of the following: 10**
- a) Compare active and passive components (two points)
 - b) Draw symbols of zener diode and LED.
 - c) List types of BJT and draw their symbols.
 - d) List specifications of resistors
 - e) Define rectifier. List different types of rectifiers.
 - f) State the applications of BJT.
 - g) State any four applications of LED.
- 5. Attempt any THREE of the following: 12**
- a) Find the value of resistor from the given colour code.
 - i) Orange, Orange, Orange, Silver
 - ii) Green, Blue, Yellow, Silver
 - b) Draw and explain working principle of half wave rectifiers and draw its waveforms.
 - c) Draw constructional diagram of LED and explain its working principle.
 - d) Explain ideal and practical voltage source with suitable diagram.
 - e) Compare CB, CC and CE configuration of transistor. (four points)

6. Attempt any TWO of the following:**12**

- a) i) Differentiate between analog and digital ICS
 - ii) List different types of resistors and capacitors.
 - b) i) Define filter and state its type.
 - ii) Draw and explain 'C' filter with suitable diagram.
 - c) i) Define the following parameter of transistor
 - 1) α
 - 2) β
 - 3) Input resistance
 - ii) Describe the working of transistor as a switch.
-