

22331

22223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Define the term calibration.
 - b) List silent features of PMMC.
 - c) Define resolution.
 - d) Give function of delay line in CRO.
 - e) List the measurements done with the help of CRO. (any four)
 - f) List types of
 - i) AC
 - ii) DC bridges
 - g) State different types of standard.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Give significance of calibration and tech steps carried out for calibration.
 - b) State the role of series resistance connected in PMMC movement.
 - c) Compare analog meter and digital meter. (any four points)
 - d) Describe with sketch the procedure to measure given unknown inductance value using relevant type of bridge.
- 3. Attempt any THREE of the following:** **12**
- a) With neat sketches give working of given type of ohm-meter.
 - b) Draw and explain each block of digital voltmeter.
 - c) With neat sketch explain frequency measurement by CRO.
 - d) Explain static and dynamic characteristics of instruments.
- 4. Attempt any THREE of the following:** **12**
- a) Convert PMMC movement into DC ammeter of the range 0 to 50mA.
 - b) Describe the following terms of voltmeter
 - i) Loading effect
 - ii) Sensitivity
 - c) Identify the parameter measured by the give instruments.
 - i) LUX meter
 - ii) LCR meter
 - iii) DFM
 - iv) DVM

Also list 2 specifications of each meter.
 - d) Determine value of R_x in Wheston's bridge if $R_1 = 400\Omega$, $R_2 = 4K\Omega$, $R_3 = 2K\Omega$.
 - e) Draw labelled diagram of function generator.

5. Attempt any TWO of the following:**12**

- a) Explain types of errors occurs in instrument.
- b) Using schering bridge, describe the procedure to measure the unknown value of capacitance.
- c) Compare dual slope DVM and SAR type DVM. (four points)

6. Attempt any TWO of the following:**12**

- a) Calculate the value of multiplier resistance on the 50V range of a DC voltmeter that uses a $200\mu\text{A}$ meter movement with an internal resistance of 100Ω .
 - b) With sketches give procedure how phase is measured by Lissajous pattern on CRO.
 - c) A DC voltmeter use $50\mu\text{A}$ and having an internal resistance of 400Ω . Calculate the value of multiplier on ranges.
 - i) 10V
 - ii) 25V
 - iii) 20V
-