

22212

22232

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

- | | Marks |
|--|--------------|
| 1. Attempt any FIVE of the following : | 10 |
| (a) Define electric current. | 2 |
| (b) State the meaning of active and passive circuit. | 2 |
| (c) State the meaning of the term dielectric strength. | 2 |
| (d) Define Magneto Motive Force. | 2 |
| (e) Define Magnetic Hysterisis. | 2 |
| (f) Define Co-efficient of coupling. | 2 |
| (g) State the formula to calculate the energy stored in a magnetic field. | 2 |
| 2. Attempt any THREE of the following : | 12 |
| (a) State the effects of electric current. Explain any one effect with a suitable example. | 4 |
| (b) Compare resistances in series and parallel. | 4 |
| (c) With suitable diagram explain the action of capacitor. | 4 |
| (d) State and explain statically and dynamically induced emfs. | 4 |



3. Attempt any THREE of the following : 12

- (a) State and explain ideal voltage source and current source. 4
- (b) An electric kettle is required to heat 0.6 litre of water from 10 °C to the boiling point in 5 minutes. Calculate the resistance of the heating element, if the supply voltage is 240 V. 4
- (c) State and explain Kirchoff's Voltage Law. 4
- (d) Enlist the types of capacitor. Explain the construction of any one. 4

4. Attempt any THREE of the following : 12

- (a) Compare direct current and alternating current. 4
- (b) Calculate the resistance between the points B & D, for the Fig. 4.1. 4

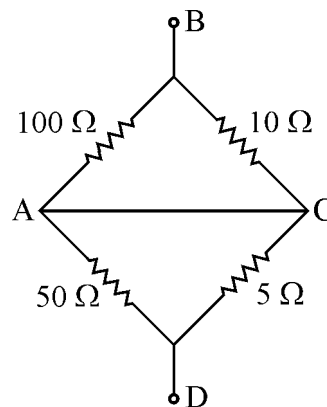


FIG. 4.1

- (c) Applying Kirchoff's voltage law, find the current flowing through the resistance 6 Ω & for the circuit shown in Fig. 4.2 4

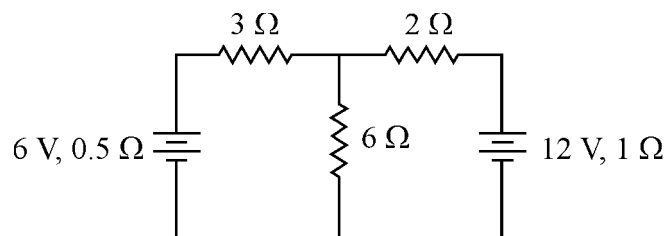


FIG. 4.2

- (d) Derive the equation for energy stored in a capacitor. 4
- (e) Three capacitors A, B and C have capacitances 10, 50, 25 μF each are connected in parallel to a 250 V supply. Calculate
- (i) Total capacitance
- (ii) Charge across each capacitor. 4
- 5. Attempt any TWO of the following : 12**
- (a) Draw the experimental setup to plot the 'B-H Curve' of a magnetic material. Explain the procedure and draw the curve. 6
- (b) An iron ring of mean length 50 cm has an air gap of 1 mm and a winding of 200 turns. If the permeability of iron is 400, calculate the field strength when a current of 2 A flows through the coil. 6
- (c) (i) State Faraday's Laws of Electro Magnetic Induction.
- (ii) Draw and explain the experimental setup to demonstrate the generation of statically induced emf. 6
- 6. Attempt any TWO of the following : 12**
- (a) Compare electric and magnetic circuit. 6
- (b) Two coils having 50 and 400 turns respectively are wound side by side on a closed iron ring of area of cross-section 100 cm^2 and mean length 200 cm. Calculate
- (i) Mutual inductance between the coils, if the relative permeability of iron is 2000.
- (ii) emf induced in the second coil, when a zero ampere current grows to 10 A in a time of 0.02 sec in the first coil. 6

22212

[4 of 4]

- (c) If a coil of 1000 turns is linked with a flux of 0.02 weber, when carrying a current of 10 A, calculate
- (i) Inductance of the coil.
 - (ii) Induced emf, if the current is uniformly reversed in the coil in 0.01 seconds.

6
