

22216

22232

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw symbol of zener diode and photo diode.
- (b) State any two applications of FET.
- (c) In BJT, what is a thermal runaway ?
- (d) Draw Transfer characteristics for N-channel depletion MOSFET and label it.
- (e) Define line and load regulation.
- (f) State the need of DC regulated power supply.
- (g) List any two applications of LED.



- 2. Attempt any THREE of the following :** **12**
- (a) Compare photo diode and LED on the basis of definition, function, type of biasing and application.
 - (b) Draw and explain input and output characteristics of CE configuration of BJT.
 - (c) Draw basic block diagram of DC regulated power supply and explain each block with output wave form.
 - (d) Explain load line concept and dc biasing of a transistor.
- 3. Attempt any THREE of the following :** **12**
- (a) Draw positive clipper circuit, explain operation with waveform.
 - (b) State necessity of filter. Draw and explain working of bridge rectifier connected with π (pi) filter with output waveform.
 - (c) A JFET has a drain current of 5 mA. If $I_{DSS} = 10$ mA and $V_{GS}(\text{off}) = -5$ V, find the value of (i) V_{as} (ii) V_p .
 - (d) Explain zener diode as a voltage regulator.
- 4. Attempt any THREE of the following :** **12**
- (a) Draw and explain the working of negative clamper with circuit diagram and waveform.
 - (b) Describe operation of voltage divider biasing with circuit diagram.
 - (c) (i) In CE config., if $\beta = 99$, $I_{CEO} = 50$ μ A. If base current is 0.5 mA, determine I_C and I_E .
(ii) Derive relation between α and β .
 - (d) Calculate input impedance of JFET if reverse gate source voltage is V and gate current is 10^{-3} μ A.
 - (e) Differentiate between Zener and Avalanche Breakdown.

5. Attempt any TWO of the following :**12**

- (a) Justify, FET is called as 'Voltage operated device.'
- (b) An AC supply of 230 V is applied to HWR through transformer with turns ratio 10 : 1. Find Avg. DC O/P voltage, current and P/V of diode and RMS voltage.
- (c) Draw and explain VI characteristics of photodiode. Also define term dark current in photo diode.

6. Attempt any TWO of the following :**12**

- (a) Differentiate PN junction and zener diode on basis of current flow, Breakdown voltage, Doping, applications.
 - (b) Compare CB, CE, CC on the basis of phase shift, voltage gain, input impedance, output resistance.
 - (c) Compare half wave and full wave bridge rectifier and centre tap rectifier on the basis of no. of diodes, ripple frequency, ripple factor, efficiency of rectifier.
-

