

22221

22232

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
 - (8) Preferably, write the answers in sequential order.

Marks

1. Attempt any FIVE of the following :

10

- (a) State KCL and KVL.
- (b) Define : (i) Cycle (ii) Time period w.r.t. sinusoidal AC waveform.
- (c) Draw Impedance triangle of R-L series A.C. Circuit.
- (d) State the relation between phase and line currents in balanced delta connected system.
- (e) State the working principle of D.C. motor.
- (f) State the application of stepper motor (any **two**).
- (g) State the types of earthing.



- 2. Attempt any THREE of the following :** **12**
- (a) Compare Electric and Magnetic Circuits (any four points)
 - (b) Draw circuit diagram, phasor diagram, waveforms of v & i and impedance triangle of R – S series A.C. circuit.
 - (c) Explain three phase e.m.f generation.
 - (d) Discuss any one speed control method of D.C. shunt motor with neat circuit diagram.
- 3. Attempt any THREE of the following :** **12**
- (a) State Fleming's right hand rule and Lenz's law.
 - (b) Derive an EMF equation of single phase transformer.
 - (c) Describe the procedure for reversal of rotation of D.C. shunt motor with neat diagram.
 - (d) Compare fuse and MCB on any four points.
- 4. Attempt any THREE of the following :** **12**
- (a) State the meaning of B.H. Curve. Draw B.H. curve for Iron Material.
 - (b) Starter is necessary for starting of three phase induction motor. Justify the statement.
 - (c) Explain working of three phase induction motor.
 - (d) Enlist type of stepper motor and servo motor.
 - (e) State the concept or function of limit switch and proximity switch.
- 5. Attempt any TWO of the following :** **12**
- (a) A $318 \mu\text{F}$ capacitor is connected across a 230 V, 50 Hz system. Determine :
 - (i) Capacitive reactance
 - (ii) Current

- (iii) Maximum current
 - (iv) Maximum voltage
 - (v) Equation of current
 - (vi) Equation for voltage
- (b) Three similar coils each of resistance of 15Ω and an inductance of 0.08 H are connected in star to the 3-phase, 400 V , 50 Hz supply system. Find the phase current, line current, phase voltage, line voltage, total phase power and total line power.
- (c) Explain the operation of universal motor with neat diagram. State the application of it.

6. Attempt any TWO of the following :

12

- (a) An inductance of 2 mH and a resistance of 50Ω are connected in series across a 230 V , 50 Hz supply mains
- Determine
- (i) Inductive reactance
 - (ii) Angular frequency
 - (iii) Impedance
 - (iv) Current
 - (v) Circuit power
- Draw circuit diagram.
- (b) Describe the maintenance procedure of the FHP motors.
- (c) Explain working of ELCB with neat diagram, also state general specifications of it.
-

