

17329

14115

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each Section on separate answer sheet.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

SECTION – I

1. Attempt any **FIVE** of the following: **20**
- a) Define the following.
 - (i) Frequency
 - (ii) Phase
 - (iii) Average value
 - (iv) Maximum value
 - b) State relation between phase and line current and voltage in balanced star and delta connections.
 - c) Give expression for e.m.f. equation, and transformation ratio of transformer.

P.T.O.

- d) Explain with suitable diagram working of capacitor start split phase induction motor.
- e) Differentiate between Fuse and MCCB. (Any four points)
- f) Describe the safty tools in order to avoid shocks.
- g) What is earthing? Why is it necessary?

2. Attempt any THREE of the following: 18

- a) With neat sketches, explain working of Auto transformer. List four specification.
- b) Explain with block diagram speed control of induction motor by variable frequency drive method.
- c) (i) State classification of drives.
(ii) List factors for selection of Motor for different drives.
- d) Draw neat sketch and explain working of ELCB.

3. Attempt any THREE of the following: 12

- a) Define voltage and current with their units.
- b) Three resistance of $25\ \Omega$ each are connected in delta across a 3- ϕ 400 V a.c. supply. Draw the circuit, find phase current, line current, line voltage, phase voltage.
- c) Define efficiency and voltage regulation of transformer.
- d) Compare squirrel cage motor with slip ring rotor of 3-phase induction motor. (Any four points)
- e) What is tariff? State the types of tariff.

SECTION – II

4. Attempt any FIVE of the following: **20**

- a) Define conductor and insulator with example. (any two)
- b) Define intrinsic and extrinsic semiconductor with suitable example.
- c) Draw block diagram of regulated power supply. State the function of each block.
- d) What is rectifier? State the need of rectifier.
- e) Explain the working of transistor as a switch.
- f) Define oscillator. State the criterial conditions for sustained oscillations.
- g) Draw symbol of NOT and XNOR gate with their truth table.

5. Attempt any THREE of the following: **18**

- a) Give comparison between CB, CE and CC configuration. (six points)
- b) Draw and explain two stage RC coupled amplifier. List two application.
- c) Draw and explain Hartley Oscillator. State its two application.
- d) What is universal gate? Design basic gates using any one of the universal gate.

6. Attempt any THREE of the following: **12**

- a) Draw symbol of the following:
 - (i) PN junction diode
 - (ii) Zener diode
 - (iii) LED
 - (iv) UJT
 - b) Give comparison between BJT and FET. (Any four points)
 - c) Draw circuit diagram of Bridge rectifier. Explain with their waveform.
 - d) Draw block diagram of OP-AMP. State function of each block.
 - e) Convert following binary number to decimal, Hexadecimal and octal form.
 $(101101.1101)_2$
-