

17323

21819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any TEN of the following:** **20**
- Define waveform and instantaneous value of an alternating quantity.
 - An alternating voltage is having maximum value 230 volt. What is its average value and rms value?
 - Define inductive reactance and capacitive reactance.
 - Define power factor and reactive power.
 - Draw a admittance triangle by considering capacitive susceptance and inductive susceptance.
 - Give any two applications of parallel resonant circuits.
 - State the relations between line and phase value of voltage and current for balanced star connected load.
 - Define phase sequence of three phase ac quantity.

P.T.O.

- i) With a neat diagram explain the concept of open circuit.
- j) Define active network and passive network.
- k) State Thevenin's theorem applied to DC circuits.
- l) Give the meaning of "Steady state condition and state the behaviour of pure C at steady state condition.

2. Attempt any FOUR of the following:

16

- a) Instantaneous expression for voltage and current are given by
 $V = 141.4\sin 314 t$, $i = 28.28\sin\left(314t + \frac{\pi}{3}\right)$.

Determine:

- i) Voltmeter and ammeter reading.
 - ii) Frequency of current
 - iii) Power factor
 - iv) Power consumed.
- b) Derive the expression for current and voltage in pure resistive circuit when connected to sinusoidal AC voltage. Draw the phasor diagram.
- c) For the given impedance triangle as shown in Figure No. 1.
- i) Identify the types of circuit.
 - ii) Mark parameters of all sides of the triangle
 - iii) State the nature of power factor
 - iv) Draw a sinusoidal waveform of voltage and current.

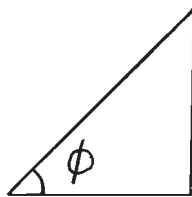


Fig. No. 1

- d) Define the impedance and draw the impedance triangle.

- e) A resistance of 100Ω and $50\mu\text{f}$ capacitor are connected in series across a 230V , 50Hz supply. Find :
- The impedance.
 - The current flowing through circuit.
 - Voltage across resistance and capacitance.
 - Power factor and power.
- f) A circuit consists of a resistance of 20Ω in series with an inductance of 95.6 mH and a capacitor of $318\mu\text{f}$. It is connected to a 500V , 25Hz supply. Find the current in the circuit and power factor.

3. Attempt any **FOUR** of the following:

16

- Compare series resonance circuit with parallel resonance circuit.
- Derive the expression for resonant frequency for the circuit as shown in Figure No. 2

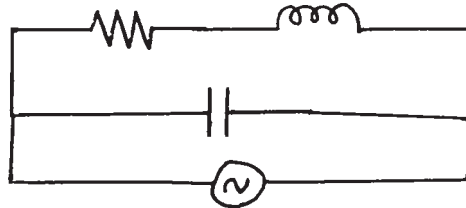


Fig. No. 2

- If $z_1 = 3 + j7$ and $z_2 = 12 - j16$ are connected in parallel. Find the equivalent impedance of combination.
- If $A = 4 + j7$, $B = 8 + j9$, $C = 5 - j6$ then calculate,
 - $\frac{A+B}{C}$
 - $\frac{A \times B}{C}$
 - $\frac{A+B}{B+C}$
 - $\frac{B-C}{A}$

- e) What is meant by independent voltage source? What are its type?
- f) A resistance of 100Ω and $50\mu\text{F}$ capacitor are connected in series across a 230V , 50Hz supply find :
- The impedance
 - The current flowing through circuit.
 - Voltage across resistance and capacitance.
 - Power factor and power.

4. Attempt any FOUR of the following:

16

- Distinguish between balanced and unbalanced load.
- State any four advantages of polyphase circuit over single phase circuit.
- A 3ϕ star connected load having $R = 15\Omega$, $L = 0.04\text{ H}$, $C = 50\ \mu\text{F}$ in each phase. It is supplied by 440V , 3ϕ , 50 Hz AC .
Find :
 - Impedance per phase (Z_{ph})
 - Line current
 - Power factor
 - Power consumed.
- Derive the formulae for delta to star transformation.
- Using mesh analysis calculate current through 10Ω resistor as shown in Figure No. 3.

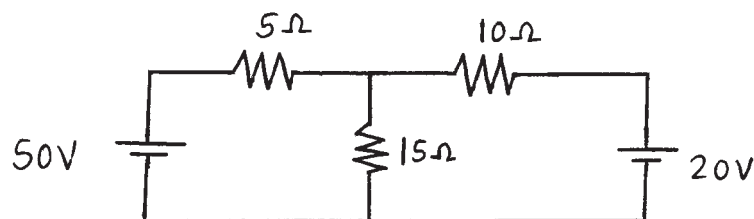


Fig. No. 3

- f) Using Nodal analysis Calculate current through 15Ω resistor as shown in Figure No. 4.

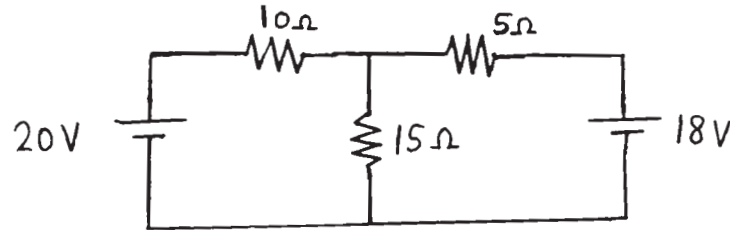


Fig. No. 4

5. Attempt any TWO of the following:

16

- a) Explain the generation of three phase emf for two pole machines. Represent them mathematical as well as graphical form.
- b) i) State Norton's theorem and write its procedural steps of find current in a branch.
ii) Find the current passing load resistance R_L as shown in Figure No. 5.

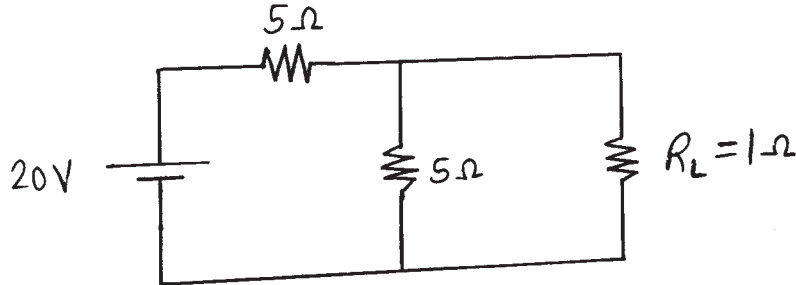


Fig. No. 5

- c) i) State superposition theorem and write its procedural steps to find current in a branch.
ii) Find the I_L for the circuit shown in Figure No. 6 using superposition theorem.

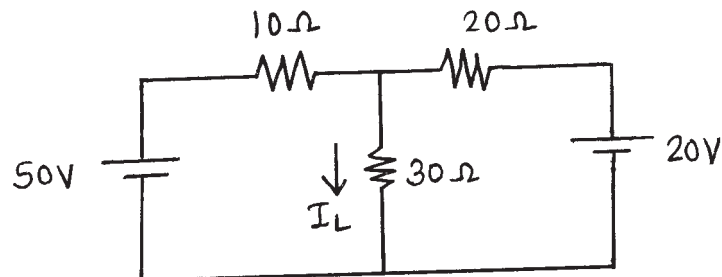
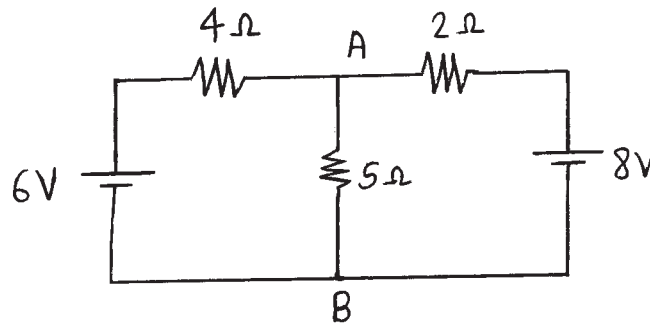


Fig. No. 6


6. Attempt any **FOUR** of the following:

16


- a) Find current through branch AB using Thevenin's theorem as shown in Figure No. 7.

**Fig. No. 7**

- b) Find the value of load resistance R_L to get maximum power transfer to it in Figure No. 8.

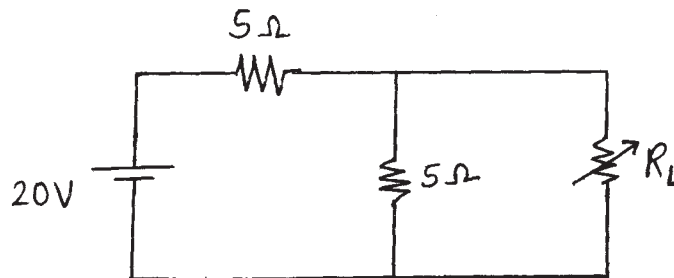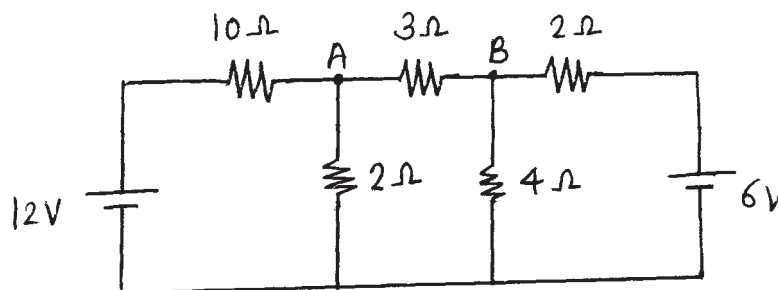**Fig. No. 8**

- c) Using Nodal voltage analysis find current through each branch in Figure No. 9.

**Fig. No. 9**

- d) Draw the curves for following parameters during series resonance condition with respect to frequency.
- i) X_L
 - ii) X_C
 - iii) I
 - iv) Z
- e) Explain the concept of initial condition and state switching circuits for the elements R, L and C.
- f) Compare single phase system with three phase system by using following points.
- i) Voltage
 - ii) Transmission efficiency.
 - iii) Size of machine to produce same output.
 - iv) Cross sectional area of conductor.
-