

17331

21819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. a) Attempt any SIX of the following:

12

- (i) Define the terms with respect to electrical circuits.
 - 1) Node
 - 2) Branch
- (ii) State Kirchoff's current law.
- (iii) Draw a parallel resistive circuit with three resistors. State the formula for equivalent resistance.
- (iv) Define form factor of sinusoidal signal. State its value.
- (v) Define three phase balanced load and unbalanced load.
- (vi) State Lenz's law.
- (vii) Explain the need of earthing.
- (ix) State the function of
 - 1) MCB
 - 2) Fuse

P.T.O.

b) Attempt any TWO of the following:

8

- (i) Write the emf equation of single phase transformer. State the meaning of each term in it.
- (ii) Draw a neat diagram of Resistance Split Phase Induction motor. State any two applications of it.
- (iii) Write any four safety precautions to be taken while working with any electrical system.

2. Attempt any FOUR of the following:

16

- a) Explain Kirchoff's Voltage Law with a suitable example.
- b) Calculate the current through $10\ \Omega$ resistors for the following circuit Fig. No. 1 by loop current method.

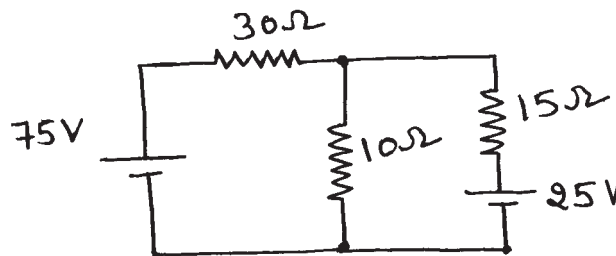


Fig. No. 1

- c) Find the value of R_{12} , R_{23} and R_{31} for the following circuit in Fig. No. 2.

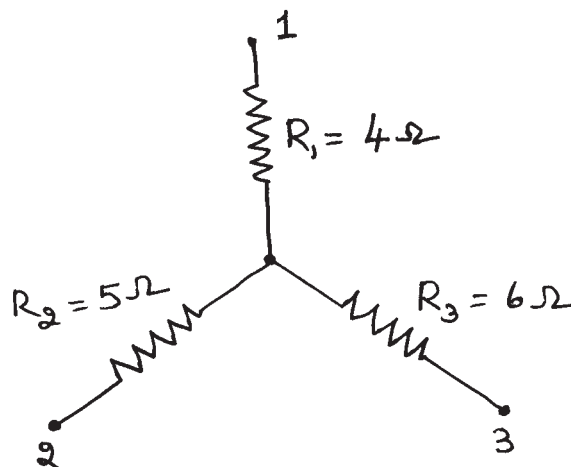


Fig. No. 2

- d) State the two types of statically induced emf with neat diagram and explain.
- e) Define power factor. State its significance.
- f) State the working principle of single phase dynamometer type wattmeter with a neat labeled diagram.

3. Attempt any FOUR of the following: 16

- a) Draw the circuit, waveform and write equations of voltage and current for a purely capacitive circuit.
- b) Draw Lag and Lead quantities with respect to sinusoidal signals. State its equations.
- c) State Faraday's law of electromagnetic induction and its application (any two) in electrical engineering.
- d) Calculate amplitude, rms value, time period and phase angle for $e = 100 \sin (314 t + 30^\circ)$
- e) Draw the voltage and current waveforms of purely resistive circuit containing 70Ω resistors, when a supply voltage of 115 V, 50 Hz is applied. Label the waveforms with amplitude and its equations.
- f) State any four advantages of 3- ϕ systems over 1- ϕ systems.

4. Attempt any FOUR of the following: 16

- a) The equivalent resistances of two resistors when connected in parallel and series are 10Ω and 45Ω respectively. Calculate their values.
- b) State the behavior of an AC circuit containing pure inductance, through equations, waveforms, phasor diagrams for voltage and current.
- c) Define active power and reactive power. Differentiates these two, based on the following:
 - (i) Equation
 - (ii) Unit of measurement
- d) Explain resonance in R-L-C series circuit.
- e) State the principle of operation of a single phase transformer with neat diagram.

- f) Define the following with respect to transformers:
- Voltage ratio
 - Transformation ratio
 - Efficiency
 - Regulation

5. Attempt any FOUR of the following:

16

- a) Given the voltage and current equations for an ac circuit.
 $V = 100 \sin (wt + 30^\circ)$ and $I = 15 \sin (wt + 60^\circ)$
 Determine:
- Phase difference
 - Power factor
 - Impedance
 - V_{rms}
- b) State relationship between voltage and current quantities in Star connected system and Delta connected system.
- c) Draw three phase circuit showing supply and star connected load. Show different line and phase quantities in it.
- d) Three similar coils each having a resistance of 20Ω and inductance of 0.05 H are connected in star to a 3- ϕ , 400 V , 50 Hz supply. Calculate:
- Line Current
 - Total power absorbed.
- e) Calculate:
- Line current
 - Phase current
 - Power factor
 - Total power for the given balanced load in Fig. No. 3.

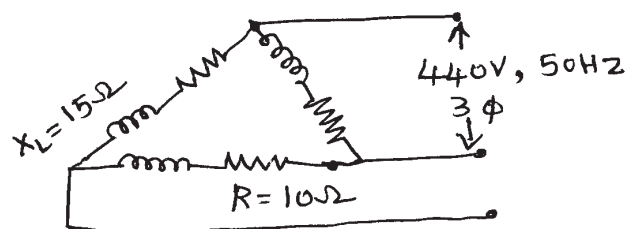


Fig. No. 3

- f) A 50 kVA, 6600 V/250 V, 1- ϕ transformer has 52 secondary turns. Find:
- No of primary turns
 - Full load primary and secondary currents.

6. Attempt any **FOUR** of the following:

16

- A coil of resistance 40Ω and 0.08 H inductance is connected to 230 V , 50 Hz supply. Find impedance, reactance, current and power factor.
- For the circuit given below in Fig. No. 4. Calculate X_L , X_C , Z and current I_{rms} .

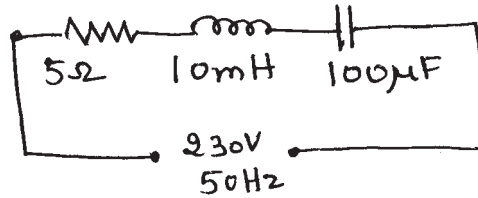


Fig. No. 4

- Three impedance of $(8 + j6)$ each are connected in star to a 3- ϕ , 440 V , 50 Hz balanced Ac supply. Calculate:
 - Line and phase voltages
 - Line and phase currents
 - Impedance
 - Power factor.
- Give any two applications of each:
 - Universal motor
 - Transformer
 - Resistance split phase induction motor
 - Capacitor start induction motor.
- Explain the reason why single phase induction motor is not self starting.
- State any four careful actions to be performed while handling shock victims.