



17213

11819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions :**
- (1) *All questions are **compulsory**.*
 - (2) *Illustrate your answers with neat sketches **wherever** necessary.*
 - (3) *Figures to the **right** indicate **full** marks.*
 - (4) *Assume suitable data, if **necessary**.*
 - (5) *Mobile Phone, Pager and any other Electronic Communication devices are **not** permissible in Examination Hall.*

Marks

1. Attempt **any ten** of the following : **20**
 - a) Compare active and passive component (any two points)
 - b) Draw the symbol of N-channel MOSFET and P- channel JFET.
 - c) Draw V-I characteristics of zener diode.
 - d) List any two types of coupling used in amplifier.
 - e) Give any two applications of P-N junction diode.
 - f) Write any two advantages and disadvantages of ICs.
 - g) List any two types of filter.
 - h) Differentiate between N-channel and P-channel J-FET.
 - i) Draw the symbol of zener diode and LED.
 - j) Give the classification of ICs.
 - k) Draw circuit diagram of P-N junction diode in forward bias.
 - l) Define resistance with its unit.

2. Attempt **any four** of the following : **16**
 - a) Enlist any four applications of electronics.
 - b) Explain working principle of LED.
 - c) Compare CE, CB, CC (any four point).
 - d) Explain working of single stage CE amplifier with circuit diagram.
 - e) Explain zener diode as a voltage regulator.
 - f) Draw the circuit diagram of crystal oscillator and give any two application.

3. Attempt **any four** of the following : **16**
 - a) Give classification of resistors and draw symbol of any two.
 - b) Explain zener breakdown and avalanche breakdown.
 - c) Explain N-channel J-FET with its transfer characteristics.

P.T.O.



- d) Compare D-MOSFET and E-MOSFET.
- e) Derive the relation between α and β .
- f) State the need of oscillator with its two applications.

4. Attempt **any four** of the following :

16

- a) Draw forward and reverse characteristics of P-N junction diode.
- b) Compare Half Wave Rectifier and Full Wave Rectifier.
- c) Define :
 - i) Q point
 - ii) DC loadline
 - iii) Need of biasing
 - iv) Current gain
- d) Draw the circuit diagram of transformer coupled amplifier.
- e) State the need of rectifier and filter.
- f) List any two advantages and disadvantages of direct coupled amplifier over RC coupled amplifier.

5. Attempt **any four** of the following :

16

- a) Define :
 - i) Knee voltage
 - ii) Reverse saturation current
- b) Explain working of bridge rectifier with the help of waveform.
- c) Draw the circuit diagram of Astable Multivibrator with any two application.
- d) Explain formation of depletion layer in P-N junction diode.
- e) Draw the circuit diagram of two stage amplifier and state the need of multistage amplifier.
- f) Write any four applications of Schottky diode.

6. Attempt **any four** of the following :

16

- a) Explain static and dynamic resistance of diode.
 - b) Draw the block diagram of regulated power supply and explain.
 - c) Compare P.N.P and N.P.N. transistor.
 - d) Draw and explain the circuit diagram of transistor as a switch.
 - e) Explain the construction of P-channel J-FET.
 - f) Define
 - i) Ripple factor
 - ii) TUF
 - iii) Efficiency of Rectifier
 - iv) PIV.
-