

17319

11819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Assume suitable data, if necessary.
  - (5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. (A) Attempt any SIX :

6 × 2 = 12

- (a) State any four applications of transistor.
- (b) Define term stability factor.
- (c) Define gain and band width.
- (d) Which type of MOSFET is called “Normally ON MOSFET” ? Why ?
- (e) Sketch the single tuned amplifier.
- (f) List the types of power amplifier.
- (g) State 2 advantages of JFET over BJT.
- (h) Define intrinsic standoff ratio.

17319

[2 of 4]

**(B) Attempt any TWO :**

**2 × 4 = 8**

- (a) Explain the operating principle of PNP transistor.
- (b) What is thermal runaway in transistor ? How it can be avoided ?
- (c) Explain how Zener diode is used as voltage regulator.

**2. Attempt any FOUR :**

**4 × 4 = 16**

- (a) Define  $\alpha$  and  $\beta$  of transistor and derive the relation between them.
- (b) Explain need of biasing. List any two methods of biasing.
- (c) With the help of diagram, explain the working of N-channel JFET.
- (d) Compare CB, CC, CE configuration (any 4 points).
- (e) Draw block diagram of voltage series and current series feedback.
- (f) Draw the functional block diagram of IC 723. Describe its working.

**3. Attempt any FOUR :**

**4 × 4 = 16**

- (a) Draw the circuit diagram for common base configuration and draw its output characteristics.
- (b) Describe source self bias method of FET with neat circuit diagram.
- (c) Draw miller sweep generator and give its two applications.
- (d) Compare the different types of coupling (any 4 points).
- (e) Draw the circuit diagram of  $-5$  V regulator using 7905 and describe its working.
- (f) Define the following : (1) Load Regulation (2) Line Regulation.

**4. Attempt any FOUR :****4 × 4 = 16**

- (a) List 4 applications of FET. Draw the drain and transfer characteristics of JFET.
- (b) Draw the diagram of single stage CE amplifier and state the function of each component.
- (c) Describe the construction, operation of E-MOSFET.
- (d) Describe class B push pull amplifier with neat circuit diagram.
- (e) Compare class A, class B and class C power amplifier on (1) position of operating point (2) efficiency (3) conduction angle (4) O/P waveform.
- (f) What is oscillator ? State applications of oscillator.

**5. Attempt any FOUR :****4 × 4 = 16**

- (a) In C.E. configuration if  $\beta = 150$ , leakage current  $I_{CEO} = 100 \mu\text{A}$  and base current in  $0.5 \text{ mA}$ , determine  $I_C$  and  $I_E$ .
- (b) State the advantages and disadvantage of crystal oscillator.
- (c) Compare small signal amplifier (voltage amplifier) and power amplifier.
- (d) Draw common source FET amplifier. Describe its operation.
- (e) Describe the working principle of UJT as relaxation oscillator with neat circuit diagram.
- (f) Draw pin diagram of IC 78XX and IC 79XX and state their features and advantages.

**P.T.O.**

**6. Attempt any FOUR :****4 × 4 = 16**

- (a) Explain with a neat circuit, voltage divider bias method for biasing a transistor.
  - (b) Draw the circuit of series transistor voltage regulator and describe its operation.
  - (c) State the meaning of positive and negative feedback.
  - (d) Draw the circuit of double tuned amplifier and sketch the frequency response.
  - (e) Draw circuit of RC phase shift oscillator and describe its working.
  - (f) Explain the construction of UJT and draw its symbol.
-