

17321

11819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any TEN of the following :

20

- (a) Draw the symbols of Schottkey-diode and Varactor diode.
- (b) Define ripple factor and PIV of HWR.
- (c) State the types of filters.
- (d) List various transistor biasing methods.
- (e) Define α and β of the transistor.
- (f) State reason BJT is called as bipolar junction transistor.
- (g) State the application of FET (any four).
- (h) Define line regulation and load regulations.
- (i) State the Barkhausen criteria of oscillations.

- (j) Sketch symbol of NAND gate and NOR gate.
- (k) Convert :
 - (i) $(AFB_2)_{16} = (?)_{10}$
 - (ii) $(43)_8 = (?)_2$
- (l) Give the different types of amplifier coupling.
- (m) Sketch output characteristics of CE configuration. Show all the regions.
- (n) State the need of biasing of BJT.

2. Attempt any FOUR of the following :

16

- (a) Describe working principle of LED with diagram.
- (b) Describe thermal runaway of transistor and explain how it can be avoided.
- (c) Compare half wave rectifier and full wave rectifier on the basis of :
 - (i) No. of diode
 - (ii) PIV
 - (iii) Ripple factor
 - (iv) Type of transformer used
- (d) Describe the functional pin diagram of regulator IC 78XX and 79XX.
- (e) Explain with circuit diagram fixed bias method of BJT.
- (f) State advantages and disadvantages of positive and negative feedback related to oscillator.

3. Attempt any FOUR of the following :

16

- (a) Describe operating principle of photo diode with neat diagram.
- (b) Explain with circuit diagram two stage transformer coupled amplifier using transistors.

- (c) Draw the circuit of centre tapped rectifier with LC filter, also draw input output waveforms.
- (d) Draw V.I. characteristics of UJT and explain its working principle.
- (e) Describe the working principle of N channel enhancement MOSFET.
- (f) Explain crystal oscillator with circuit diagram.

4. Attempt any FOUR of the following :

16

- (a) Draw VI characteristics of P-N junction diode in forward and reverse bias. Define static and dynamic resistance.
- (b) Explain with circuit diagram transistorised shunt voltage regulator.
- (c) Compare CB and CE configurations w.r.t.
 - (i) input resistance
 - (ii) output resistance
 - (iii) current gain
 - (iv) voltage gain
- (d) Describe the emitter biasing technique of BJT with ckt. diagram.
- (e) Draw and explain the circuit diagram of class A push pull amplifier.
- (f) Define terms :
 - (i) Drain resistance
 - (ii) Mutual conductance
 - (iii) Amplification factor
 - (iv) Pinch off voltage of FET

P.T.O.

5. Attempt any FOUR of the following :**16**

- (a) Draw circuit diagram of direct coupled amplifier and explain function of each component.
- (b) State applications of FET and MOSFET.
- (c) Describe the working of transistor as a switch with neat circuit diagram.
- (d) Describe working of Hartley oscillator with neat diagram.
- (e) Explain how zener diode is used as voltage regulator.
- (f) State applications of digital electronics.

6. Attempt any FOUR of the following :**16**

- (a) Draw & explain construction of point contact diode.
 - (b) Define terms w.r.t. transistor.
 - (i) DC load line
 - (ii) operating point
 - (c) Draw block diagram of DC regulated power supply and state function of each block.
 - (d) Compare BJT and FET (any 4 points).
 - (e) Describe Ex-OR gate. Draw its symbol and truth table.
 - (f) Draw circuit diagram of colpitts oscillator, colpitts oscillator has $C_1 = 250 \text{ PF}$, $C_2 = 100 \text{ PF}$ and $L = 60 \mu\text{H}$. Find the value of frequency of oscillation.
-