

17322

11819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
 - (7) Use of steam tables, logarithmic, Mollier's chart is permitted.

Marks

1. Attempt any FIVE :

20

- (a) Define measurement and state the significance of electrical measurement system.
- (b) List three advantages & one disadvantage of PMMC instrument.
- (c) Draw the labelled diagram of dynamometer type wattmeter showing its construction.
- (d) Draw the connection diagram of one wattmeter method to measure active power in three phase circuit. State one limitation of this method.
- (e) List four main parts of operating mechanism of induction type energy meter.
- (f) Classify the resistances from the point view of measurements.
- (g) What is CRO ? List three uses of it.

[1 of 4]

P.T.O.

2. Attempt any FOUR :**16**

- (a) Compare PMMC & MI instruments on the basis of :
 - (i) suitability
 - (ii) power consumption
 - (iii) scale
 - (iv) cost
- (b) Draw the labelled diagram of PMMC instrument.
- (c) List four electrical effects used in measuring instruments.
- (d) List three torques used in analog instruments. Also state the function of any one torque.
- (e) Define :
 - (i) accuracy
 - (ii) precision
 - (iii) sensitivity
 - (iv) reproducibility
- (f) List four advantages of electronic instruments over other instruments.

3. Attempt any FOUR :**16**

- (a) Draw the connection diagram of voltmeter & ammeter to measure voltage & current in single phase ac circuit.
- (b) Draw the labelled diagram of MI attraction type instrument.
- (c) PMMC instrument is not suitable to measure AC. Why ?
- (d) State the reason for :
 - (i) PMMC instrument has linear scale
 - (ii) MI instrument has non-linear scale.
- (e) A PMMC instrument gives full scale deflection of 5 mA when a voltage of 50 mV is applied across it. Calculate :
 - (i) Value of R_{sh} for full scale deflection of 50 A.
 - (ii) Value of R_s for full scale deflection of 500 V.
- (f) A 1 mA PMMC meter with internal resistance of 100Ω is to be converted into 100 mA ammeter. Calculate value of shunt resistance required.

4. Attempt any FOUR :

16

- (a) Draw the impedance triangle for
 - (i) R-L circuit
 - (ii) R-C circuit
- (b) Explain the meaning of multiplying factor of wattmeter. Why it is required ?
- (c) Define active, reactive & apparent power stating their equations with units.
- (d) Explain how the range of wattmeter can be extended.
- (e) Explain the effect of power factor on wattmeter reading in two wattmeter method for (i) unity p.f. (ii) zero p.f.
- (f) In case of active power measurement in 3-phase ckt by two wattmeter method :
 - (i) Draw the connection diagram
 - (ii) State the formula for active & reactive power
 - (iii) List two advantages
 - (iv) If one wattmeter reads 2000 W & other reads 1500 watt, calculate power factor of load.

5. Attempt any FOUR :

16

- (a) (i) Draw the connection diagram of dynamometer type wattmeter showing measurement of power in single phase AC circuit.
 - (ii) Draw the connection diagram of measurement of reactive power in 3 phase circuit by one wattmeter method.
- (b) (i) Define electrical energy & state its unit.
 - (ii) Draw the circuit diagram to calibrate single phase energy meter by direct loading.
- (c) (i) Draw the block diagram of digital energy meter.
 - (ii) List two advantages of digital energy meter over induction type energy meter.
- (d) (i) Draw the labelled connection diagram of 1-phase induction type energy meter.
 - (ii) What is creeping in energy meter ? State any remedy by which it can be avoided.
- (e) Explain with diagram simple V-I method to measure medium resistance.
- (f) Draw connection diagram of earth tester to show its construction.

P.T.O.

6. Attempt any FOUR :**16**

- (a) Explain how megger can be used for measurement of high resistances.
 - (b) Compare analog multimeter v/s digital multimeter on
 - (i) accuracy
 - (ii) power requirement
 - (iii) cost
 - (iv) portability
 - (c) Draw the connection diagram of Weston type of frequency meter.
 - (d) Explain with diagram working of phase sequence indicator.
 - (e) State the function of synchroscope. Also state the purpose of synchronizing.
 - (f) Explain the use of function generator.
-