



17329

11819

3 Hours / 100 Marks

Seat No.

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

- Instructions :** (1) *All questions are compulsory.*
(2) *Answer each Section on separate answer sheet.*
(3) *Illustrate your answers with neat sketches wherever necessary.*
(4) *Figures to the right indicate full marks.*
(5) *Assume suitable data, if necessary.*
(6) *Use of Non-programmable Electronic Pocket Calculator is permissible.*
(7) *Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.*

Marks

SECTION – I

1. Attempt **any nine** of the following :

18

- Define power and energy with their units.
- Draw a 3-phase delta connected supply system.
- State the relationship between
 - Line current and phase current
 - Line voltage and phase voltage for 3-phase star connection.
- Write the working principle of transformer.
- Define the following terms for 3-phase I.M.
 - Slip
 - Synchronous speed.
- Write classification of drives with example.
- What is the function of MCCB and fuse ?

P.T.O.



- h) State applications of any four safety tools used in electrical workshop.
- i) Write specification and rating of 3-phase autotransformer.
- j) Define the following terms related to AC fundamentals.
- i) Phase
 - ii) RMS value.
- k) Write down the equation to find out the active power in 3-phase system. State the meaning of each term.
- 2. Attempt any four of the following :** **16**
- a) Explain the concept of voltage and current. Write its unit.
 - b) Three resistors of 50 ohm are connected in delta across a 400 volt, 3-phase, 50 Hz A.C. supply. Calculate the line current, phase current, line voltage and phase voltage.
 - c) Derive the EMF equation of a single phase transformer.
 - d) Draw the torque-speed characteristics of 3-phase I.M. and explain the nature.
 - e) Draw neat constructional sketch of single phase autotransformer. State its two applications.
- 3. Attempt any four of the following :** **16**
- a) Why earthing is essential in electrical installation ? State types of earthing.
 - b) Explain star-delta starter for 3-phase induction motor with diagram.
 - c) Define the terms :
 - i) Transformation ratio
 - ii) Current ratio
 - iii) Voltage ratio
 - iv) Turns ratio.
 - d) List the enclosures and mountings used for electrical drives.
 - e) State any four safety precautions to be taken while handling an electrical equipments.
 - f) Explain construction and working principle of sodium vapour lamp.



SECTION – II

4. Attempt **any nine** of the following : 18
- a) Define insulator and conductor with two examples of each.
 - b) Draw the symbol of zener diode and state its two applications.
 - c) Define filter and rectifier.
 - d) List four applications of amplifier.
 - e) State the universal gates with its symbol.
 - f) Convert $(0.8)_{10}$ to equivalent binary.
 - g) Draw symbols of NPN and PNP transistors.
 - h) State two ideal characteristics of operational amplifier.
 - i) State the working principle of photo diode.
 - j) Draw the labelled symbol of OP-AMP.
 - k) Convert $(11100)_2$ to equivalent decimal.
5. Attempt **any four** of the following : 16
- a) Explain construction and working of PN junction diode. Also draw symbol of PN junction diode.
 - b) Draw and explain zener diode as a voltage regulator.
 - c) With the help of a neat diagram explain the working and characteristics of photo transistor.
 - d) Draw and explain non-inverting configuration of an OP-AMP.
 - e) Draw circuit diagram of two stage RC coupled amplifier.
 - f) Draw the logic symbol and construct the truth table for each of the following :
 - i) Two input OR gate
 - ii) Three input AND gate.



6. Attempt **any four** of the following :

- a) Draw and explain block diagram of regulated power supply.
 - b) Explain Hartley oscillator with diagram.
 - c) Explain OP-AMP as subtractor.
 - d) Draw and explain circuit diagram of single stage CE amplifier.
 - e) Explain bridge fullwave rectifier with circuit diagram and waveform.
 - f) Draw logic symbol and truth table of following gate :
 - i) NAND
 - ii) XNOR.
-