

17415

11819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any TEN of the following:

20

- a) State the function of commutator in DC generator and name the material used for commutator.
- b) Draw a neat connection diagram of dc short shunt differential compound generator showing the direction of all the currents.
- c) State Fleming's Left Hand Rule.
- d) State any four application of DC shunt motor.
- e) A DC shunt motor operating on a supply voltage of 200 V dc has armature resistance of 0.5Ω . If it's armature current is 25A then calculate back emf.
- f) State the function of overload coil and No. volt coil in dc motor starter.
- g) State any four characteristics of core type transformer.

P.T.O.

- h) A 100 KVA transformer has iron loss of 3 KW on full load. Calculate its iron loss at 50% of full load.
- i) State and justify which of the following two transformer is better.
Transformer A = 4% voltage regulation
Transformer B = 6% voltage regulation
- j) Define all day efficiency of transformer.
- k) Why phasing out and polarity test is carried out on three phase transformer?
- l) State different types of cooling system used for three phase transformer.

2. Attempt any FOUR of the following:

16

- a) Derive the E.M.F. equation of DC generator.
- b) A 4 pole, Lap wound DC shunt generator has 1230 armature conductor. Calculate flux developed per pole. If the terminal voltage of generator is 220 V and it is driven at 1500 rpm. The armature is delivering a current of 120 A and has resistance of 0.5Ω .
- c) Explain concept of back emf in DC machine. State how it governs armature current?
- d) Explain with suitable diagrams armature diverter method and armature voltage control method for speed control of DC series motor.
- e) With the help of neat diagram, explain in brief the working of brushless DC motor.
- f) A dc series motor runs at 600 rpm taking 100 A from 230 V supply. Armature and series field winding resistances are 0.12Ω and 0.03Ω . Calculate the speed when current has fallen to 50A. Assume flux to be directly proportional to field current.

3. Attempt any FOUR of the following:**16**

- Give detail classification of transformer.
- Derive the emf equation of a transformer.
- A single phase transformer has 400 primary and 800 secondary turns. The net cross - sectional area of the core is 40 cm^2 . If the primary winding is connected to 50 Hz supply at 500 V Calculate:
 - Peak value of the flux density in the core.
 - Voltage induced in secondary.
- Explain why rating of a transformer is in KVA and not in KW?
- A single phase transformer with ratio of 500/200 V takes a no load current of 3A at 0.4 p.f. lagging. If secondary supplies a current of 50A at a p.f 0.85 lagging, estimate the current taken by primary.
- OC test is performed on L.V. winding and SC test is performed on H.V. winding of transformer. Justify.

4. Attempt any FOUR of the following:**16**

- Performance of a transformer is analyzed on all day efficiency. Justify the statement.
- A 20 KVA, 1000/400V, single phase 50 Hz transformer has iron and full load copper losses as 300 watt and 500 watt respectively calculate:
 - Efficiency at full load and 0.8 P.F. lagging.
 - Efficiency at half load and unity P.F.
- A 1000 kVA single phase transformer has full load copper and iron losses as 9 KW and 7 KW respectively. During a day of 24 hours, it is loaded as given below.

Sr. No.	No. of hours	Loading	P.F.
1	6	800 KW	0.8
2	10	600 KW	0.75
3	04	200 KW	0.8
4	04	00 KW	—

Calculate the all day efficiency.

P.T.O.

- d) Explain polarity test on single phase transformer.
- e) State condition of parallel operation of transformer.
- f) For a 3 KVA, 220/110 V, 50 Hz 1 ϕ transformer, draw a experimental set up to conduct direct loading test on it. Determine the range of instruments to be used for the direct loading test.

5. Attempt any FOUR of the following:

16

- a) List various losses in a transformer. State their location. State method to minimize these losses.
- b) Two 1 ϕ transformer with equal turns have impedances of $(0.5 + j3) \Omega$ and $(0.6 + j10) \Omega$ w.r.t. secondary. If they operate in parallel determine. How they will share a load of total 100 KW p.f. of 0.8 lagging?
- c) Explain with neat diagram the procedure of conducting phasing out test on 3 ϕ transformer.
- d) Explain with neat diagram open delta connection of 3 ϕ transformer.
- e) For Delta - star connection of 3 ϕ transformer:
 - (i) Draw the connection diagram
 - (ii) List any two advantages of this connection
 - (iii) State the area of application.
- f) State criteria for selection of distribution transformer.

6. Attempt any FOUR of the following:

16

- a) Explain with neat diagram construction of three phase auto transformer.
 - b) Compare single phase auto transformer with two winding transformer. (any four points)
 - c) Draw a neat circuit diagram of connection of CT and PT in power measurement circuit also explain its working.
 - d) Describe working of welding transformer.
 - e) What is the most important precaution while operating a C.T.
 - f) Explain construction and working of isolation transformer.
-