

# 17563

**11819**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any TEN of the following:** **20**
- a) Give two examples of active components and passive components.
  - b) Determine the value of resistance for given color code :  
Red, Red, Orange.
  - c) State different types of capacitors.
  - d) Give two examples of trivalent and pentavalent impurities.
  - e) Draw Pin Diagram of IC-741.
  - f) Draw circuit diagram of Inverting Amplifier.
  - g) Draw symbol of PNP and NPN transistor.
  - h) Draw symbol of LDR and Photodiode.

P.T.O.

- i) List different types of temperature sensors.
- j) Draw labelled diagram of optocoupler.
- k) Give detailed classification of type of control system.
- l) What is combined loop system.
- m) Convert the following.
  - (i)  $(28)_{10} = (?)_2$
  - (ii)  $(39)_{10} = (?)_2$
- n) Draw symbol and truth table for NAND gate.

**2. Attempt any FOUR of the following:**

**16**

- a) Define resistor. Draw its symbol and write its formula.
- b) Compare conductor and insulator with suitable example.
- c) Draw diagram and waveform for full wave rectifier and explain its working.
- d) Explain how LVDT is used for displacement measurement using suitable diagram.
- e) Explain closed loop control system and how it differ from open loop system.
- f) Differentiate Analog and Digital electronics.

**3. Attempt any FOUR of the following:**

**16**

- a) List different types of Inductors and state the property of Inductor.
- b) Draw V-I characteristics of forward biased and reversed biased PN - Junction diode.
- c) Draw and explain capacitive sensor for level measurement.
- d) State the applications of tensile testing sensor in Textile Industry.
- e) Compare ROM and RAM (4-points)
- f) Using NOR-gate draw -
  - (i) OR - gate
  - (ii) NAND - gate

- 4. Attempt any FOUR of the following:** **16**
- a) Draw and explain the working of transistor as a switch.
  - b) Explain active and saturation region of transistor with help of graph.
  - c) Compare RTD and Thermistor. (4-points).
  - d) Explain construction and working of Bourdon Tube.
  - e) Explain working of SR-Flip-Flop with logic circuit.
  - f) Draw Architecture of 8051- $\mu$ c (block diagram)
- 5. Attempt any FOUR of the following:** **16**
- a) Explain P&N - Type semiconductor.
  - b) State need of bridges in signal conditioning.
  - c) Explain PLC with block diagram.
  - d) Describe 3-bit up counter (asynchronous) with diagram and waveform.
  - e) Explain the working of yarn evenness tester.
  - f) Explain the mechanism of automatic weft straightening.
- 6. Attempt any FOUR of the following:** **16**
- a) Explain the virtual ground concept using circuit diagram.
  - b) What is strain gauge, state its principle and its applications.
  - c) State 2 - Applications of open loop control system and closed loop control system.
  - d) Write features of 8051 - microcontroller.
  - e) State working principle of card auto leveller, state its 2 - Applications.
  - f) Explain in brief tensile testing method.
-