

22221

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.
  - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) Define permeability and give its unit.
- (b) Define the term power factor. State its value for purely resistive circuit.
- (c) Define impedance and state its unit.
- (d) Write two possible phase sequences for a 3 $\phi$  system.
- (e) State the material used for winding and brushes in DC motor.
- (f) List any two applications of brushless DC motor.
- (g) State function of limit switch and proximity switch.

**2. Attempt any THREE of the following :**

**12**


- (a) Write formula for self and mutual inductance. Write meaning of each term in it.



22221

[2 of 4]

(b)

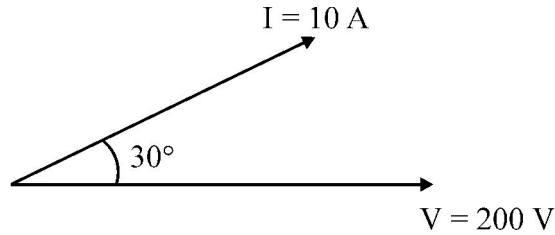

**Fig. 1**

Find :

- (i) impedance
  - (ii) power factor
  - (iii) nature of pf
  - (iv) power; from the phasor diagram shown in Fig. 1.
- (c) A  $1\phi$ , 230/115 V, 1 kVA transformer has 100 turns on secondary. Find
- (i) Number of turns on primary
  - (ii)  $I_1$  &  $I_2$
- (d) List four applications each of
- (i) DC shunt motor
  - (ii) DC series motor

**3. Attempt any THREE of the following :**

**12**

- (a) Draw a neat circuit for –
  - (i) series magnetic circuit
  - (ii) parallel magnetic circuit
- (b) Draw a circuit diagram of  $3\phi$  star connected load. Label  $I_p$ ,  $I_L$ ,  $V_p$ ,  $V_L$  on it.
- (c) For a  $3\phi$  Induction Motor write –
  - (i) two main parts
  - (ii) two types
  - (iii) two starters
  - (iv) two applications
- (d) For a MCB, state –  
purpose, rating, one advantage and one application.

## 4. Attempt any THREE of the following :

12

- (a) Find current through
- $6\Omega$
- resistor of Fig. 2 using Kirchhoff's laws.

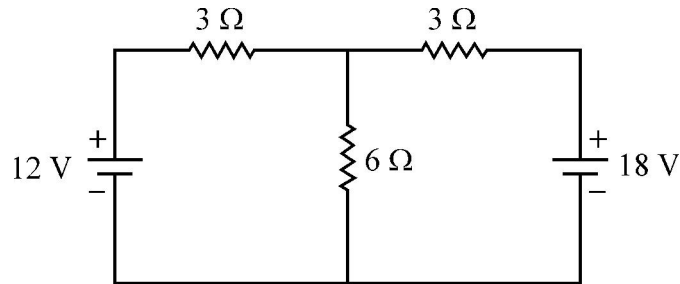


Fig. 2

- (b) With neat sketch explain speed control of DC shunt motor by flux control method.
- (c) Draw schematic diagram of  $3\phi$  Induction motor. Explain its principle of operation.
- (d) Write major four steps of maintenance procedure for FHP motors.
- (e) List any four methods of reducing earthing resistance.

## 5. Attempt any TWO of the following :

12

- (a) For a purely capacitive circuit, draw –
- circuit diagram
  - waveform for V, I
  - phasor diagram for V, I
  - write equation of current
  - state nature of pf; and
  - give value of power consumed
- (b) For a transformer, write –
- any two types;
  - any two losses;
  - any two applications.
- (c) With neat sketch explain principle of operation of a universal motor. Give two applications of the same.

**6. Attempt any TWO of the following :****12**

- (a) A resistance of  $12\Omega$  is connected in series with an inductance of 0.1 H. A 200 V, 50 Hz,  $1\phi$  supply is connected across the combination. Draw the circuit diagram and find –
- (i)  $X_L$
  - (ii)  $Z$
  - (iii)  $I$
  - (iv) pf; and
  - (v)  $P$
- (b) For a shaded pole induction motor
- (i) Draw the schematic diagram
  - (ii) Write principle of operation; and
  - (iii) give any two applications.
- (c) State purpose of earthing. State any two types of earthing. Write major four points about construction of plate earthing.
-