

22225

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw symbols of Capacitor and Inductor. State their units.
- (b) Define filter and state need of filter.
- (c) Define (i) P/V (ii) Rectification efficiency.
- (d) Define operating point (Q point) of a transistor.
- (e) Draw symbol of N-channel JFET.
- (f) Draw constructional diagram of Piezo-electric transducer and label it.
- (g) State the difference between active transducer and passive transducer (any 2 points).



2. Attempt any THREE of the following : 12

- (a) Determine the value of resistance for the following colour code :
 - (i) Green yellow orange gold
 - (ii) Red violet brown gold
- (b) Draw a neat diagram of bridge rectifier. Draw input & output waveform.
- (c) Sketch the constructional diagram of LED & describe its working.
- (d) Explain the working of NPN transistor with the help of constructional diagram.

3. Attempt any THREE of the following : 12

- (a) Explain the working of P-channel JFET with suitable diagram.
- (b) Explain :
 - (i) Seebeck effect
 - (ii) Peltier effect
- (c) Differentiate between CE & CB on the basis of
 - (i) Input resistance
 - (ii) Output resistance
 - (iii) Current gain
 - (iv) Voltage gain
- (d) Sketch input and output V-I characteristics of CE configuration and label various regions on characteristics.

4. Attempt any THREE of the following : 12

- (a) With suitable diagram, explain the working of photodiode.

- (b) Draw the block diagram of regulated power supply and explain its working.
- (c) Compare BJT and FET (any four).
- (d) In full wave bridge rectifier $V_m = 10\text{ V}$, $R_L = 10\text{ k}\Omega$, find out V_{DC} , I_{DC} , ripple factor and P/V.
- (e) Explain the working of transistor as a switch.

5. Attempt any TWO of the following :

12

- (a) Calculate peak to peak amplitude, frequency and wavelength of waveform shown in fig (a) and fig (b).

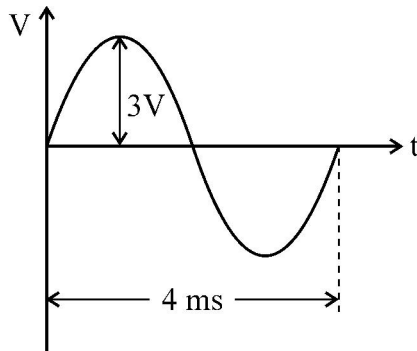


Fig. (a)

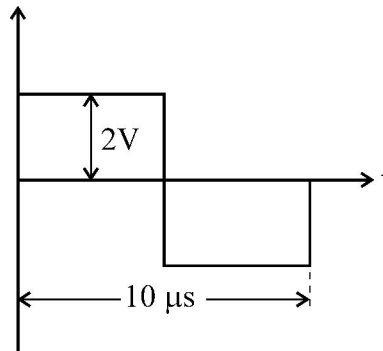


Fig. (b)

- (b) (1) Compare half wave rectifier and centre tapped full wave rectifier based on given parameter.
- P/V
 - Rectification efficiency
 - Ripple factor
 - DC voltage
- (2) State applications of zener diode (any two).
- (c) (i) Define α & β . Explain the relation between α and β .
- (ii) In NPN transistor, $I_{CEO} = 100\text{ }\mu\text{A}$, $\beta = 50$, $I_B = 20\text{ }\mu\text{A}$. Find collector current (I_C) and emitter current (I_E).

6. Attempt any TWO of the following :

12

(a) The following readings were obtained from the experiment of JFET :

$$V_{GS} \quad 0V \quad 0V \quad -0.5V$$

$$V_{DS} \quad 6V \quad 12V \quad 12V$$

$$I_D \quad 10 \text{ mA} \quad 10.2\text{mA} \quad 9.4 \text{ mA}$$

Determine :

- (i) Ac drain resistance,
 - (ii) Trans-conductance
 - (iii) Amplification factor
- (b) Identify the circuit shown in fig. (a) and explain it in brief.

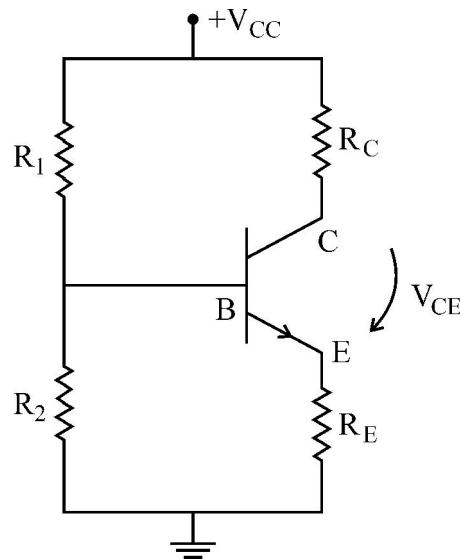


Fig. (a)

- (c) List four types of electrical pressure transducer and describe working of any one of it.
-