

# 22310

**23124**

**3 Hours / 70 Marks**

Seat No. 

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Answer each section on separate answer Book.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

## SECTION - I

1. Attempt any SIX of the following: 12
- a) Define
    - i) MMF
    - ii) Permiability
  - b) Define the term cycle and frequency.
  - c) Draw sinusoidal waveform and show the various quantities associated with it.
  - d) Draw the power triangle. State its significance.
  - e) State two applications of shaded pole motor.
  - f) Define FHP motor.
  - g) Define transformation ratio of transformer.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Compare magnetic and electric circuit. (four points)
  - b) Draw a balanced 3 phase star connected load. Show various line and phase quantities on it. Also write relationship between line and phase values of voltage and current.
  - c) Derive the emf equation of single phase transformer.
  - d) Explain the working of autotransformer. State its any two applications.
  - e) Explain construction of single phase motor with working principle.
- 3. Attempt any TWO of the following:** **12**
- a) Explain self induced emf and mutually induced emf.
  - b) Explain the working of single phase transformer.
  - c) A capacitor of  $30\mu\text{F}$  is connected in series with resistor of  $120\Omega$ . The circuit supplied with AC supply of  $230\text{V}$ ,  $50\text{HZ}$ . Determine :
    - i) Capacitive reactance
    - ii) Impedance
    - iii) Current
    - iv) Circuit power
    - v) Power factorDraw circuit diagram.

### SECTION - II

- 4. Attempt any FIVE of the following:** **10**
- a) Draw the symbol of resistor and capacitor. State its units.
  - b) List different types of electronic components with examples.
  - c) State the need of filter circuit in rectifier circuit. State its types.
  - d) Define PIV and ripple factor.
  - e) Draw the symbol of PNP and NPN transistor.
  - f) Draw the diagram showing the operating regions of transistor.

- 5. Attempt any THREE of the following:** **12**
- a) Compare Analog and Digital IC's.
  - b) Find the values of resistor from the given colour code
    - i) Orange, Red, Brown, silver
    - ii) Green, Orange, orange, silver
  - c) Explain the working of PN junction diode with suitable diagram.
  - d) Explain the construction of LED with suitable diagram.
- 6. Attempt any TWO of the following:** **12**
- a) Explain ideal and practical current source with suitable diagram.
  - b) Explain the full wave bridge rectifier with  $\pi$  filter. Draw its circuit diagram and wave form.
  - c) Explain the working of transistor as an amplifier, with suitable diagram.
-