

22323

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE of the following :


10

- (a) Define following terms :
 - (1) Fan in
 - (2) Power dissipation
- (b) Define following terms :
 - (1) Minterm
 - (2) Maxterm
- (c) List the difference between level triggering and edge triggering.
- (d) Draw symbol and truth table of
 - (1) AND gate
 - (2) NOR gate
- (e) Identify the use of Index Register, Base Pointer and Instruction Pointer.
- (f) List any four features of 8086.
- (g) List any four addressing modes of 8086 and give one example of each.



- 2. Attempt any THREE of the following :** **12**
- (a) Convert the following :
- (i) $(105)_{10} = (?)_2$ (ii) $(126)_8 = (?)_{16}$
- (b) Explain rules to simplify Boolean expression using K-map.
- (c) Draw and explain the working of D flip flop with truth table.
- (d) Implement basic gates using NAND gate only.
- 3. Attempt any THREE of the following :** **12**
- (a) Interpret De Morgan's theorem with its statement & proof.
- (b) Describe any four logical instructions with example.
- (c) Describe JK flip flop with its truth table and logic diagram.
- (d) Design half adder using K-map and basic gates.
- 4. Attempt any THREE of the following :** **12**
- (a) Write 8086 assembly language program with algorithm to add two 16 bit numbers.
- (b) Simplify following equation using K-map and realize expression using basic gates
 $f(A, B, C, D) = \Sigma m (1,3,4,5,7,9,11,13,15)$.
- (c) Differentiate between sequential and combinational circuits (4 points).
- (d) Describe pipelined architecture concept of CISC, which helps in improving system throughput.
- 5. Attempt any TWO of the following :** **12**
- (a) Interpret the given program and specify the o/p for following situations :
- MOV AX, 3459 H
MOV BX, 3A69 H
- (i) Masking of lower nibble of AX
- (ii) Rotate right through carry contents of BX by 4 positions
- (iii) Shift left contents of BX by 6 positions
- (iv) XOR AX, BX

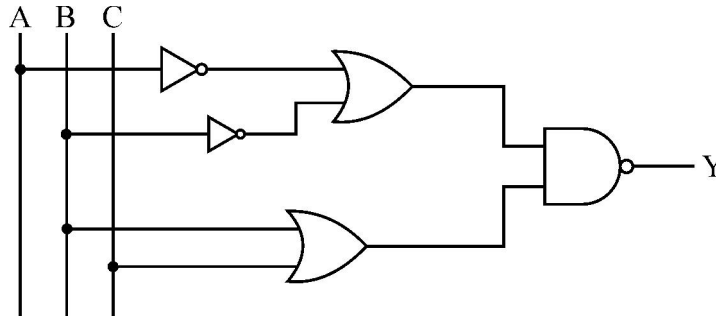- (b) Refer given figure and write the o/p for each of the following input :



A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

- (c) Draw maximum mode configuration of 8086 and explain any four control signal generated by bus controller.

6. Attempt any TWO of the following :

12

- (a) Calculate the physical address of following :

- (1) 4370 H : 561 E H
- (2) 7 A 32 : 6028 H

Also explain the process of calculating the physical address.

- (b) Design 32:1 Mux using 8:1 mux

- (c) Identify the addressing mode for the following instruction :

- (1) MOV AL, [3000 H]
- (2) Add AL, [BX + 04]
- (3) MOV AX, [BX + SI]
- (4) MOV BX, 0354 H
- (5) MOV AL, BL
- (6) MOV AX, [BX + SI + 04]

