

22331

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Define the following:–
 - i) Precession
 - ii) Resolution.
 - b) Draw circuit diagram of universal shunt in DC ammeter.
 - c) State two uses of spectrum analyzer.
 - d) List one example of time domain and frequency domain instrument.
 - e) List any four features of logic analyzer.
 - f) i) Classify the following bridges :–
 - (1) Hay bridge
 - (2) Schering bridge.ii) State one application of above bridge circuit.
 - g) Draw the circuit of Maxwell bridge.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Describe gross error, systematic error and write one source of these error.
 - b) State the reason for ammeter never connected in shunt across source of emf.
 - c) State the formula for frequency and phase measurement using Lissajous pattern on CRO with necessary diagram.
 - d) Compare series type and shunt type ohm-meter.
- 3. Attempt any THREE of the following:** **12**
- a) A 1 mA, PMMC meter movement with an internal resistance of 100Ω is to be converted into 0 - 100 mA. Calculate the value of shunt resistance.
 - b) Draw the block diagram of basic spectrum analyzer and heterodyne type spectrum analyzer.
 - c) Write specifications of DMM or logic analyzer.
 - d) Draw the block diagram of dual trace CRO and state the function of ALT/CHOP mode.
- 4. Attempt any THREE of the following:** **12**
- a) Design a multirange DC ammeter using basic movement with an internal resistance $R_m = 50\Omega$ and full scale deflection current $I_m = 1\text{mA}$. The range required are 0 - 10mA, 0 - 50mA
 - b) Draw the circuit diagram of half wave rectifier type AC voltmeter (Ideal and practical circuit diagram) and explain the function of additional component in practical circuit.
 - c) Explain the working of successive approximation type DVM.
 - d) Explain the function of grid and final anode in CRT.
 - e) Draw and explain time base generator circuit.
 - f) i) Draw block diagram of DSO.
ii) State two advantages of DSO over analog dual trace CRO.

5. Attempt any TWO of the following:**12**

- a) i) Write the meaning of absolute instrument and secondary instrument. Write one example of each one.
- ii) Define any two dynamic characteristics.
- b) i) Digital voltmeter is having $3\frac{1}{2}$ digit display.
- (1) Calculate the resolution.
- (2) Find the value displayed on this meter when unknown voltage, $V = 3.5427$ volts and the range is $0 - 10V$.
- ii) Draw the diagram of Lux meter.
- c) Explain the operation of Ramp type DVM with block diagram and waveform.

6. Attempt any TWO of the following:**12**

- a) Draw the block diagram of logic analyzer. List the modes or types of display in it.
- b) Draw the block diagram and explain Digital LCR-Q meter.
- c) i) List the detectors used in AC and DC bridges.
- ii) In an AC bridge, arms contains following constants –
- arm AB – $R = 1\text{ k}\Omega$,
- arm BC – unknown inductor coil.
- arm CD – $R = 1\text{ k}\Omega$.
- arm DA – $R = 470\Omega$ $C = 0.22\mu\text{F}$.

Calculate the unknown constants.
