

# 22423

**23124**

**3 Hours / 70 Marks**

Seat No.

--	--	--	--	--	--	--	--

- 
- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following :** **10**
- a) Define operational amplifier parameters
- i) Input bias current
- ii) Slew rate
- b) Draw and explain sign changer circuit using op-amp.
- c) List four specifications of ICLM324.
- d) State four applications of Instrumentation amplifier.
- e) State two merits of active filter over passive filter.
- f) Define with respect to filter
- i) Q-Factor
- ii) Pass band
- g) State the features of IC-555.

P.T.O.

- 2. Attempt any THREE of the following :** **12**
- a) Draw block diagram of OP-AMP and state function of each block.
  - b) List the ideal characteristics of op-amp with their ideal values. Any four.
  - c) Draw the neat circuit diagram of first order high pass filter and explain its operation.
  - d) Explain the block diagram of phase locked loop.
- 3. Attempt any THREE of the following :** **12**
- a) Sketch the circuit diagram of closed loop non-inverting amplifier and derive expression for its gain.
  - b) Draw only circuit diagram of Instrumentation amplifier using three op-amp. Write its output equation.
  - c) Explain circuit diagram of logarithmic amplifier using Op-amp.
  - d) Sketch the astable multivibrator using IC-555 and explain it.
- 4. Attempt any THREE of the following :** **12**
- a) Compare open loop and close loop configuration on the following basis
    - i) Circuit diagram
    - ii) Gain
    - iii) Bandwidth
    - iv) Applications
  - b) Design the circuit to get output voltage  $V_0 = 3V_1 + 2V_2$  where  $V_1$  and  $V_2$  are input voltages.
  - c) Sketch first order Butterworth low pass filter with component values at cut-off frequency of 12 KHz with passband gain of 2.
  - d) Explain phase shift oscillator using IC 741 with neat diagram.
  - e) Explain the working of PLL as frequency multiplier using block diagram.

5. Attempt any TWO of the following :

12

- Draw a circuit diagram of V to I converter with floating load. Derive expression for its output. List any two applications.
- Explain Schmitt trigger circuit using op-amp and how UTP and LTP are calculated.
- Design second order Butterworth high pass filter of cut-off frequency  $10 \text{ KHz}$ . Draw circuit with component values.

6. Attempt any TWO of the following :

12

- Draw inverting summing amplifier and derive the expression for its output.
- Explain the function of sample and hold circuit by using op-amp.
- From circuit diagram given in Fig. No. 1 identify the name of the circuit and calculate cut-off frequency and pass band gain.

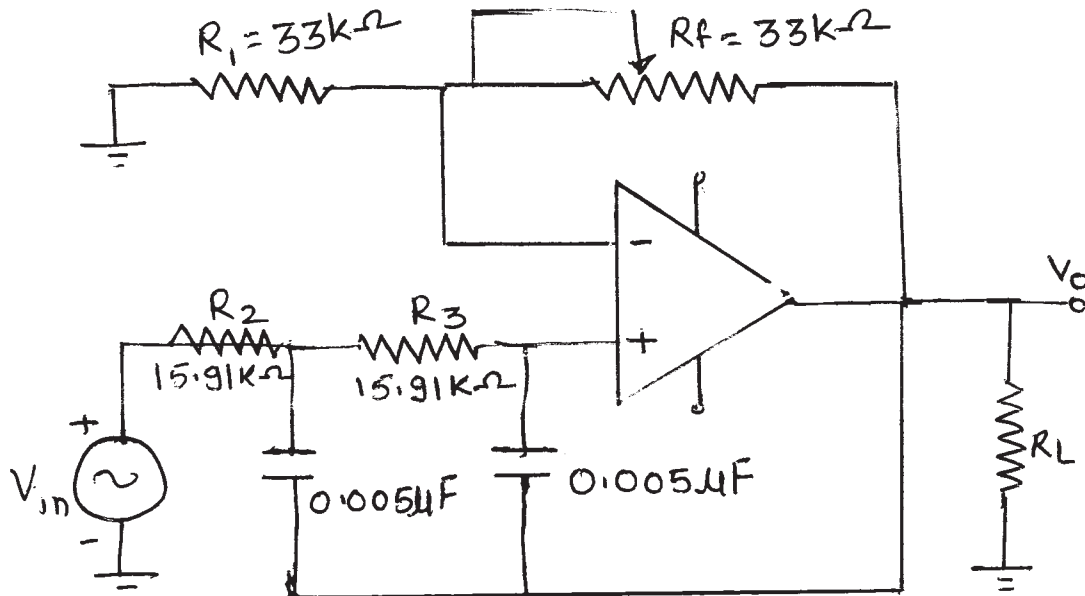


Fig. No. 1